



UNIVERSITÀ
DEGLI STUDI DI TRIESTE

lia
dipartimento
di ingegneria
e architettura


14 - VHDL Synthesis

A.Carini – Progettazione di sistemi elettronici


Synthesis

- It is an automatic method for passing from description at a high abstraction level to a description at a lower abstraction level.
- Current synthesis tools translates an RTL (register transfer level) description into a *gate level netlist*, i.e. into an interconnection of macro-cells at gate level. The models for these cells are included in *technology libraries*. Synthesis tools have a technology library for each supported technology.

Synthesis

 

RTL description

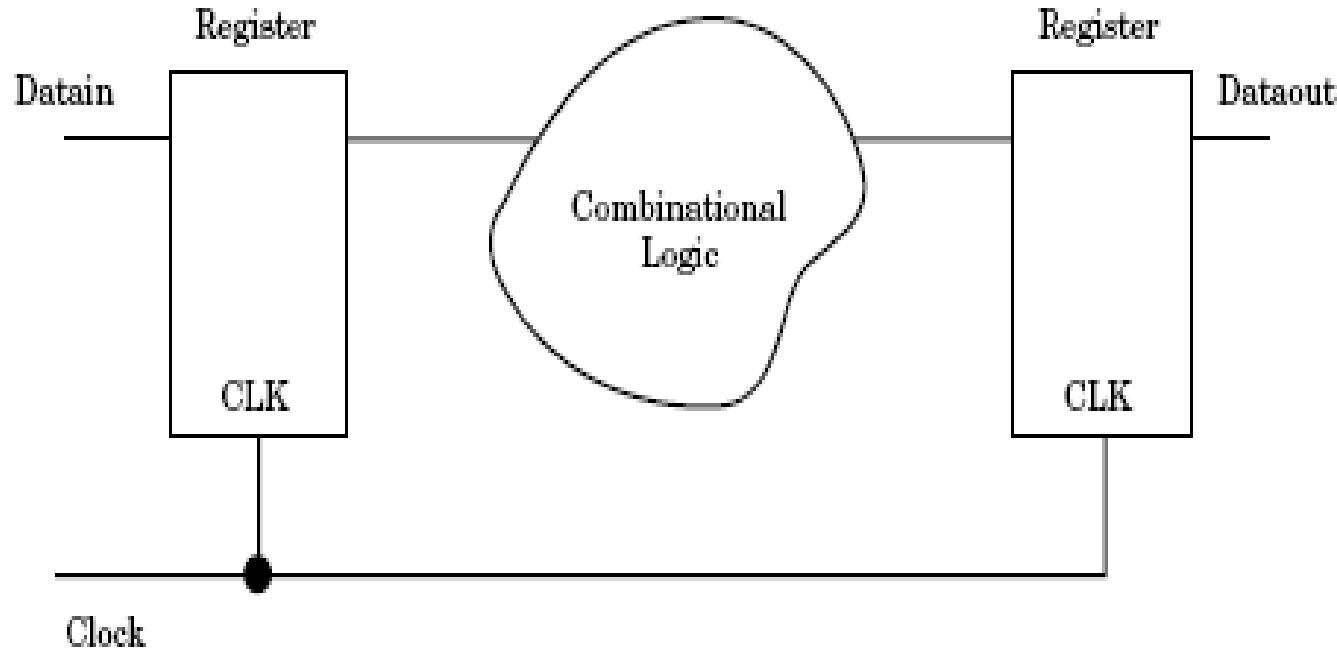

Example of RTL description

```
ENTITY datadelay IS
  PORT( clk, din, en : IN BIT;
        dout : OUT BIT);
END datadelay;


ARCHITECTURE synthesis OF datadelay IS
  COMPONENT dff
    PORT(clk, din : IN BIT;
         q,qb : OUT BIT);
  END COMPONENT;
  SIGNAL q1, q2, qb1, qb2 : BIT;
BEGIN

  r1 : dff PORT MAP(clk, din, q1, qb1);
  r2 : dff PORT MAP(clk, q1, q2, qb2);

  dout <= q1 WHEN en = '1' ELSE
    q2;

END synthesis;
```

Example of RTL description

 

Example of RTL description

```
ENTITY datadelay IS
    PORT( clk, din, en : IN BIT;
          dout : OUT BIT);
END datadelay;

ARCHITECTURE inference OF datadelay IS
    SIGNAL q1, q2 : BIT;
BEGIN
    reg_proc: PROCESS
    BEGIN


        WAIT UNTIL clk'EVENT and clk = '1';

        q1 <= din;
        q2 <= q1;


    END PROCESS;

    dout <= q1 WHEN en = '1' ELSE
                  q2;
END inference;
```


Gate level description

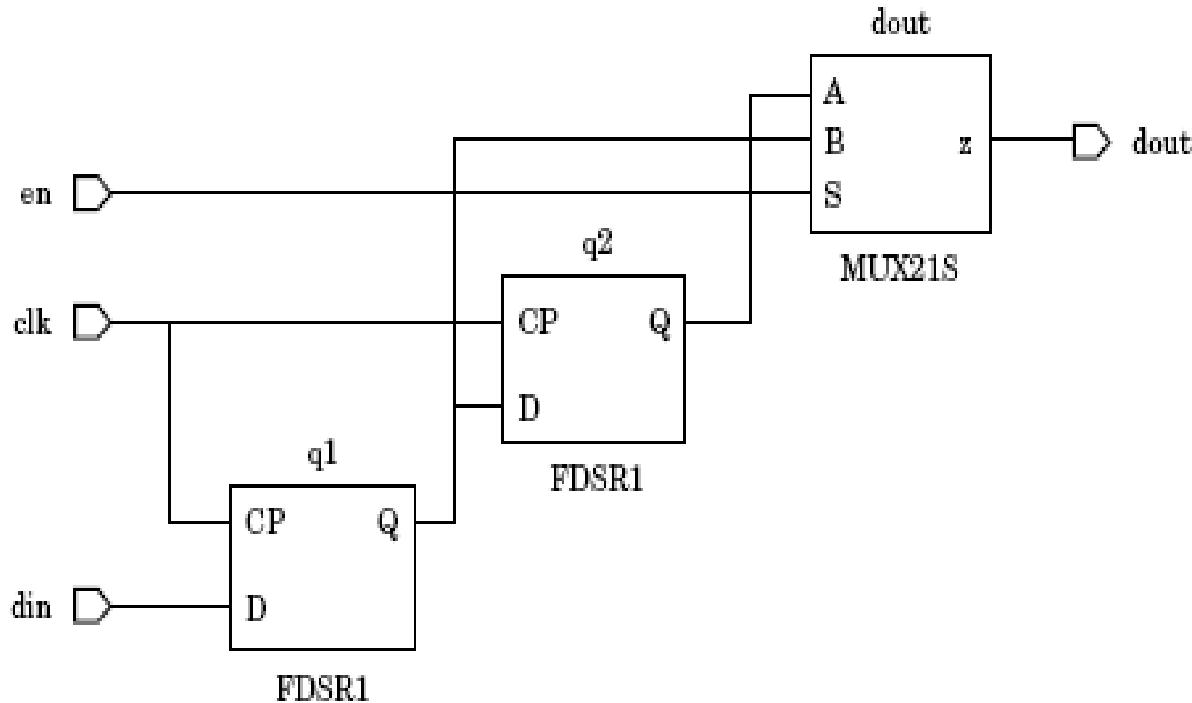

Constraints

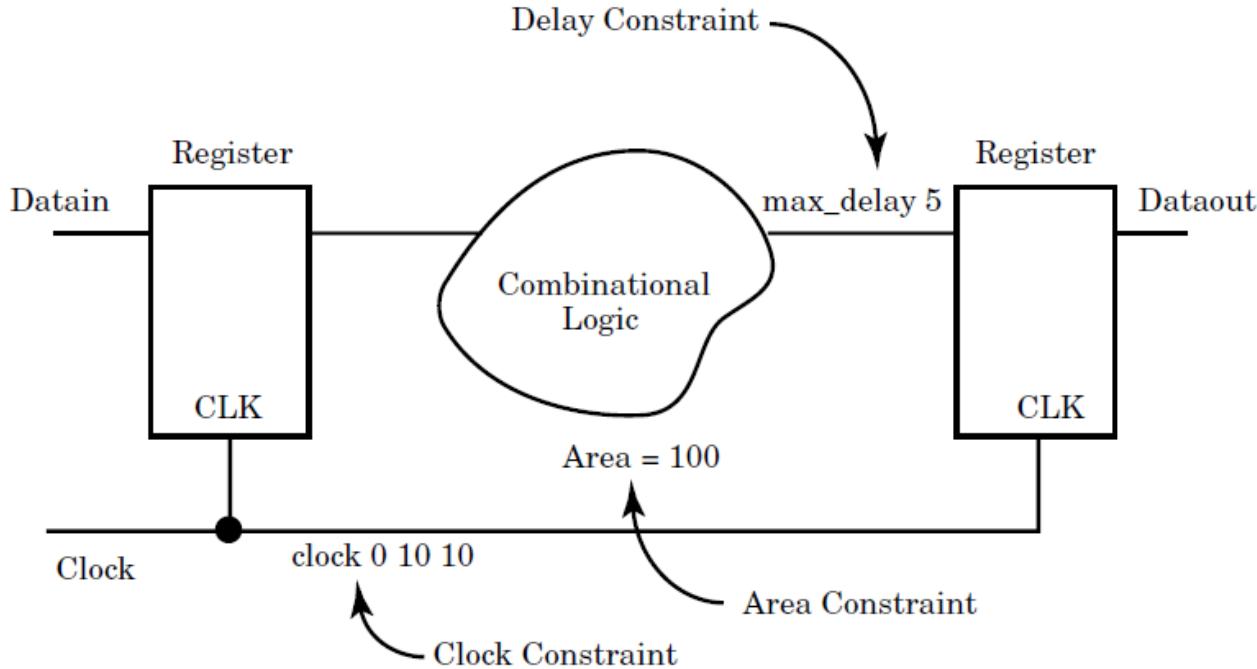

Attributes

 

Technology libraries

- Contain the information necessary for creating an hardware *netlist* for the design, given the desired logic behavior of the system.
- Contain the information useful to the synthesis process for doing the right choices in building the design.
- Contain not only the logic function of the macro-cells, but also information on the area of the cell, on the input to output delays, on every constraint on fan-out, etc.


Technology libraries example

A 2 input AND gate in the Synopsys .lib format:


```
library (xyz) {
cell (and2) {
    area : 5;
    pin (a1, a2) {
        direction : input;
        capacitance : 1;
    }
    pin (o1) {
        direction : output;
        function : "a1 * a2";
        timing () {
            intrinsic_rise : 0.37;
            intrinsic_fall : 0.56;
            rise_resistance : 0.1234;
            fall_resistance : 0.4567;
            related_pin : "a1 a2";
        }
    }
}
```

Typical delay estimation
 
`intrinsic_delay + loading_delay + wire_delay + slope_delay`



Typical delay estimation

 

Boolean optimization

- For example, by *flattening* and *factoring*.
- The unoptimized boolean description is translated in a low level description similar to that of a PLA (sum of products).
- Then, an optimization algorithm try to reduce the generated logic by sharing common terms (i.e., by introducing intermediate variables).

Flattening

Original equations
a = b and c;
b = x or (y and z);
c = q or w;

a = (x and q) or (q and y and z) or (w and x) or (w and y and z);

- Typically a fast implementation.
- Nevertheless, it could also be slower than an implementation with more logic levels, because of the high load on the input drivers.
- It requires a large area occupation.

Factoring

$$\begin{aligned}x &= a \text{ and } b \text{ or } a \text{ and } d; \\y &= z \text{ or } b \text{ or } d;\end{aligned}$$
$$\begin{aligned}x &= a \text{ and } q; \\y &= z \text{ or } q; \\q &= b \text{ or } d;\end{aligned}$$

- Surely the most efficient solution from the area viewpoint.
- It may not be the optimal solution from the delay viewpoint.
- Generally, a compromise is done:
 - Flattening on critical paths.
 - Factoring on all other paths.

Mapping to gates


- The mapping process takes the optimized logic description, the *technology library*, the user constraints and it generates an optimized network, built entirely by cells of the technology library.
- During the mapping process the cells implement the optimized logic function.
- The cells themselves are optimized for meeting the speed and area constraints.
- As final step, the synthesis tool verifies that no technology rule has been violated (e.g., the maximum fan-out of every cell, etc.)

Mapping to gates


```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.std_logic_unsigned.ALL;
ENTITY adder IS
    PORT( a,b : IN std_logic_vector(7 DOWNTO 0);
          c : OUT std_logic_vector(7 DOWNTO 0)
        );
END adder;

ARCHITECTURE test OF adder IS
BEGIN
    C <= a + b;
END test;
```

Ripple carry adder

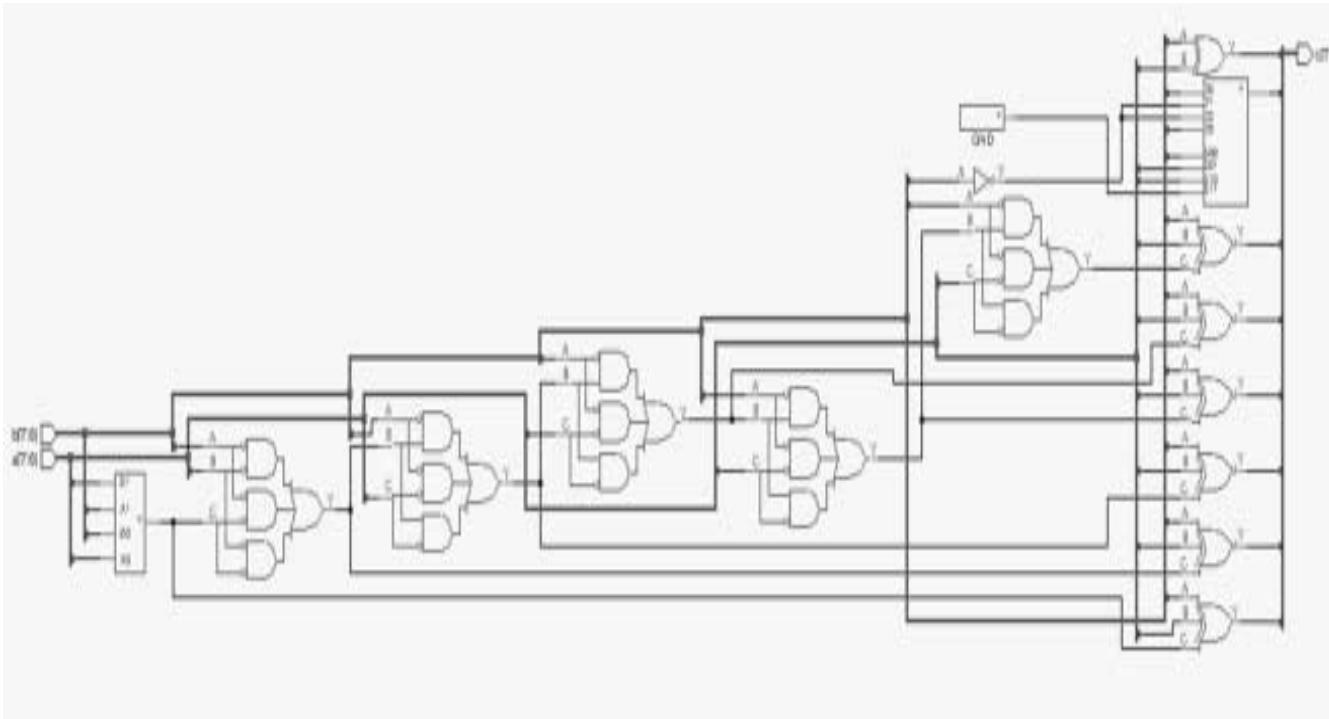

Look ahead adder

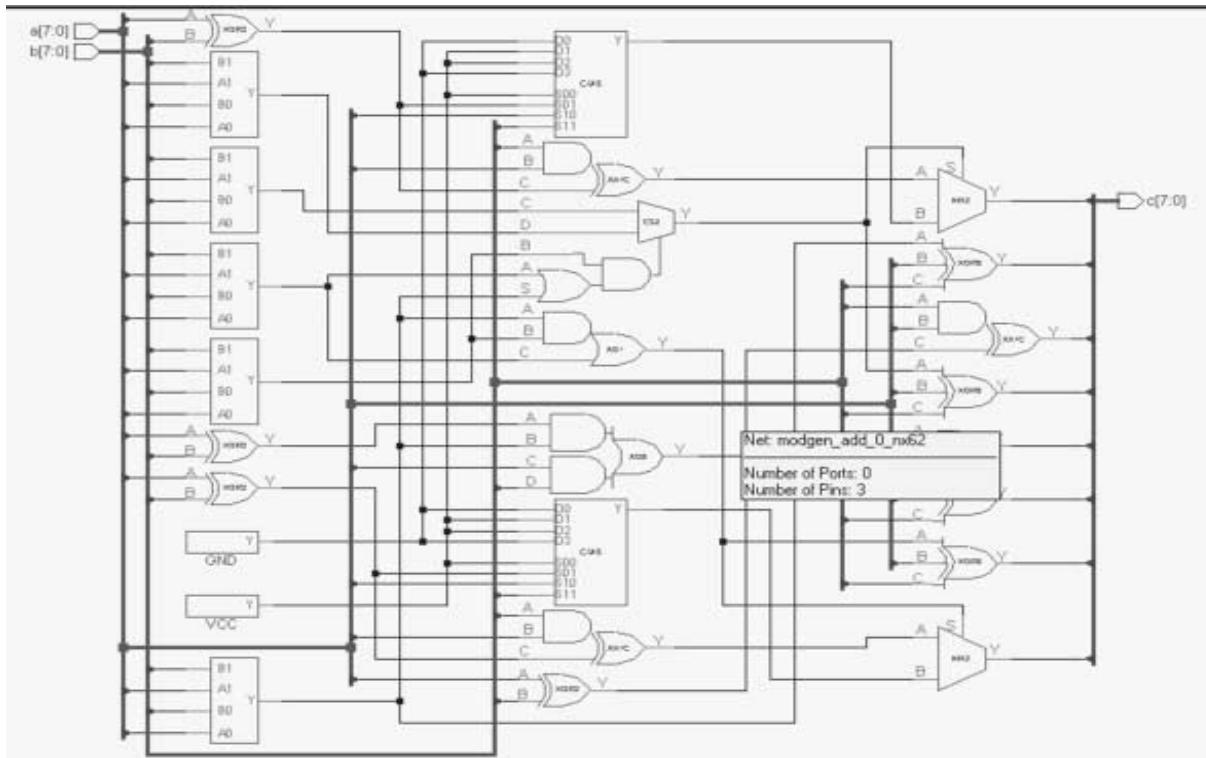

See:

- Douglas L. Perry, «VHDL programming by example» McGraw Hill,
 - Chapter 9