
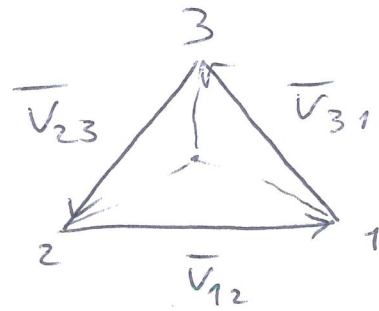


TRIFASE 1

1)

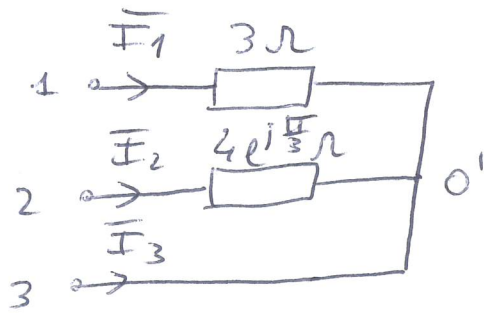

$$V_e = 240 \text{ V}$$



$$\bar{I}_1 = \frac{-\bar{V}_{31}}{3} = \frac{-240 e^{j\frac{2}{3}\pi}}{3} = -80 e^{-j\frac{2}{3}\pi} \text{ A}$$

$$\bar{I}_2 = \frac{\bar{V}_{23}}{4 e^{j\frac{\pi}{3}}} = \frac{240 e^{-j\frac{2}{3}\pi}}{4 e^{j\frac{\pi}{3}}} = 60 e^{-j\pi} = -60 \text{ A}$$

$$\bar{I}_3 = -\bar{I}_1 - \bar{I}_2 = 80 e^{j\frac{2}{3}\pi} + 60 = 20 + j69 \text{ A}$$

TRIFASE 1

2)

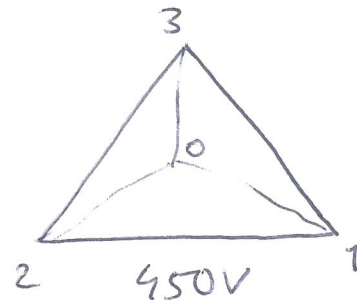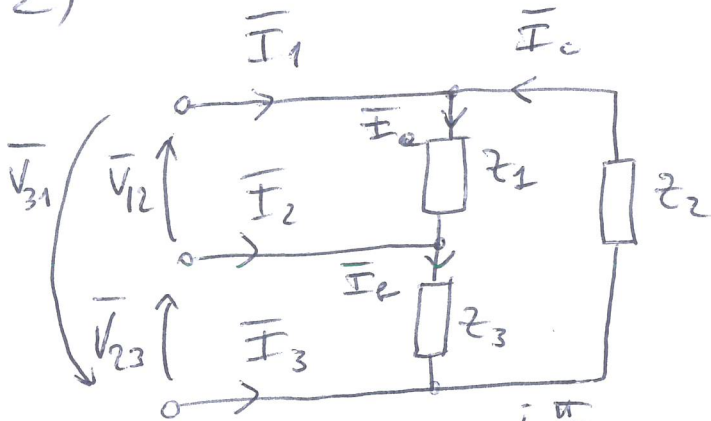

$$z_1 = 5e^{j\frac{\pi}{18}} \Omega$$

$$z_2 = 9e^{j\frac{\pi}{6}} \Omega$$

$$z_3 = e^{j\pi\frac{4}{9}} \Omega$$

$$\bar{I}_1 = \underbrace{\frac{\bar{V}_{12}}{z_1}}_{\bar{I}_a} - \underbrace{\frac{\bar{V}_{31}}{z_2}}_{\bar{I}_c} = 450 \left(\frac{1}{5e^{j\pi/18}} - \frac{e^{j\frac{2}{3}\pi}}{9e^{j\frac{\pi}{6}}} \right) =$$



$$= 450 (0.2 - j0.15) \text{ A}$$

$$\bar{I}_2 = \bar{I}_b - \bar{I}_a = \frac{\bar{V}_{23}}{z_3} - \frac{\bar{V}_{12}}{z_1} = 450 (-1.14 + j0.38) \text{ A}$$

$$\bar{I}_3 = \bar{I}_c - \bar{I}_b = \frac{\bar{V}_{31}}{z_2} - \frac{\bar{V}_{23}}{z_3} = 450 (0.94 - 0.23j) \text{ A}$$

TRIFASE 1

3/

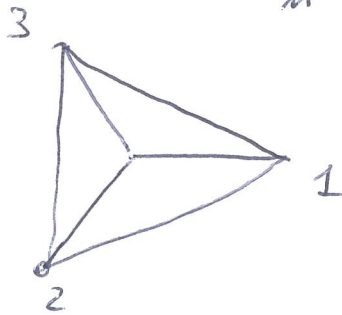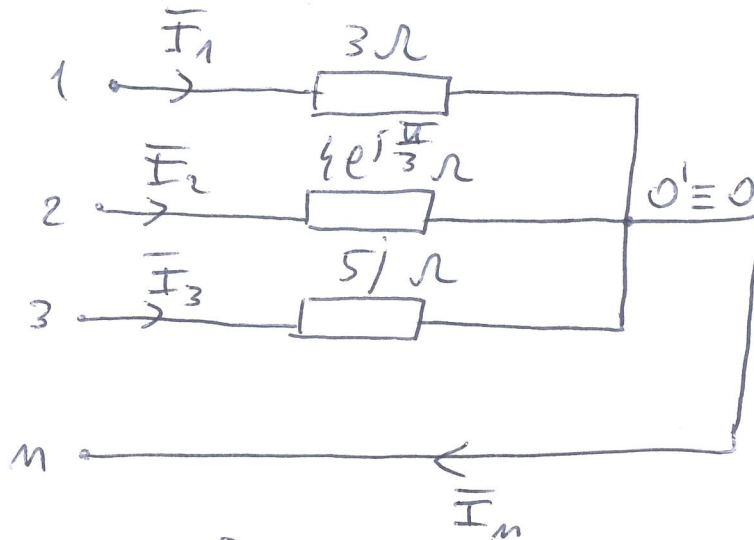

$$V_e = 240V$$

$$E_f = \frac{240}{\sqrt{3}} = 139V$$

$$\bar{I}_1 = \frac{\bar{E}_1}{z_1} = 46A$$



$$\bar{I}_2 = \frac{\bar{E}_2}{z_2} = \frac{139e^{-j\frac{2}{3}\pi}}{4e^{j\frac{\pi}{3}}} = 35e^{-j\pi} = -35A$$

$$\bar{I}_3 = \frac{\bar{E}_3}{z_3} = \frac{139e^{j\frac{2}{3}\pi}}{5j} = 28e^{j\frac{\pi}{6}}A$$

$$\bar{I}_n = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 35 + 14jA$$

TRIFASE 1

6)

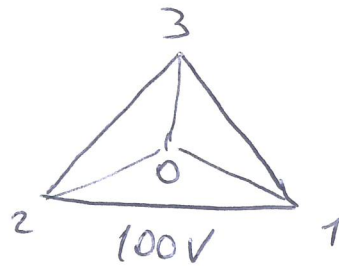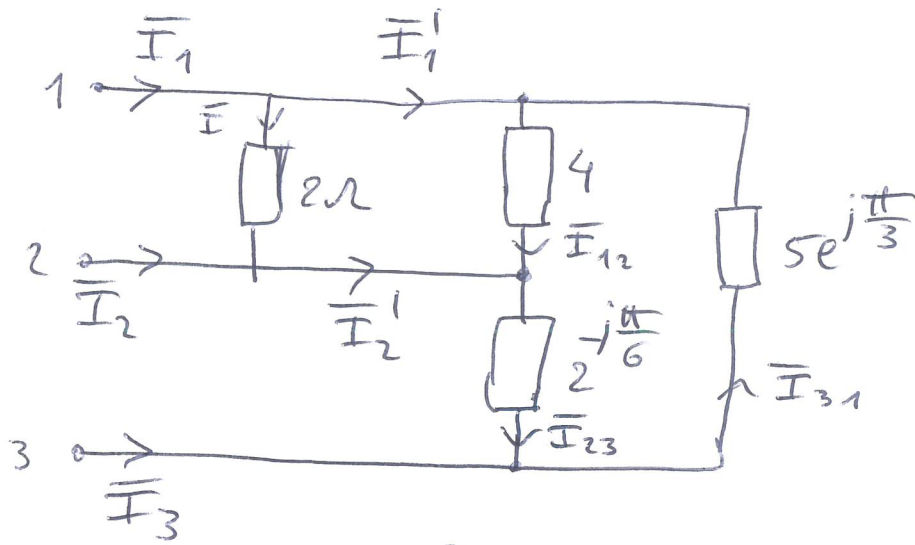


$$\begin{aligned} \bar{I}_1' &= \bar{I}_{12} - \bar{I}_{31} = \frac{100}{4} - \frac{100e^{j\frac{2}{3}\pi}}{5e^{j\frac{\pi}{3}}} = \\ &= 25 - 20e^{j\frac{\pi}{3}} = \\ &= 15 - j17.32 \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_1 &= \bar{I}_1' + \bar{I} = \frac{100}{2} + 15 - j17.32 = \\ &= 65 - j17.32 \text{ A} \end{aligned}$$

TRIFASE 1

7)

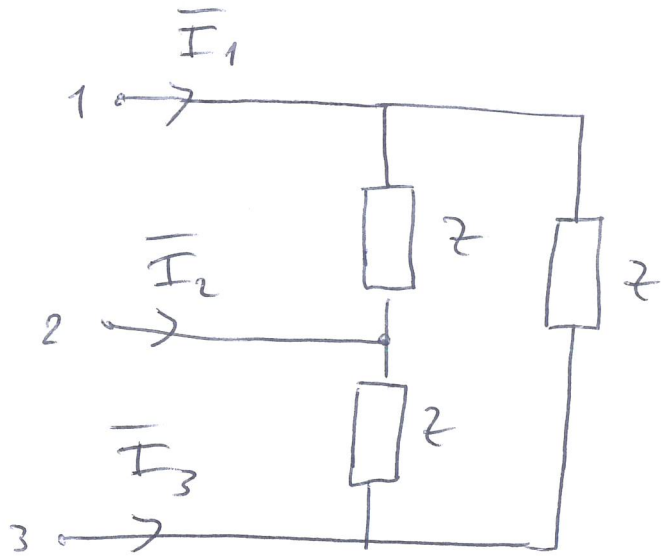



$$Z = 3 + 4j \Omega$$

$$220V \ 3\phi$$

$$|Z| = 5 \Omega$$

$$\varphi = 0.927 \text{ rad}$$
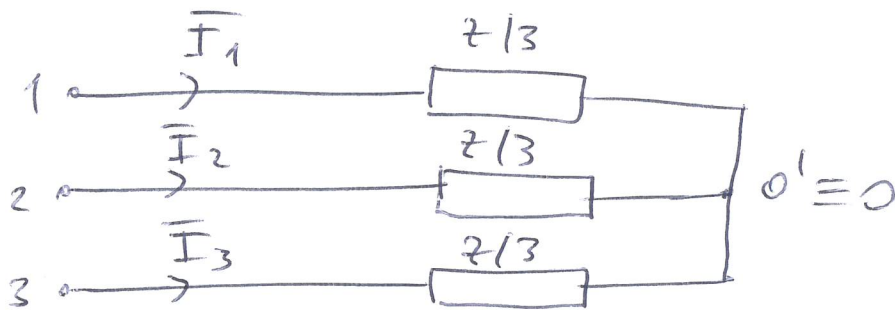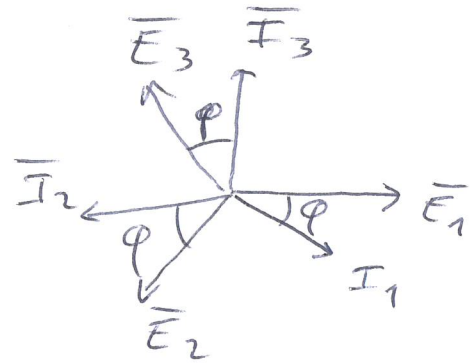
$$E_f = \frac{220}{\sqrt{3}} = 127 \text{ V}$$



$$\left| \frac{Z}{3} \right| = \frac{5}{3} \Omega$$


$$I_e = \frac{E_e}{|Z/3|} = \frac{220}{\sqrt{3} \cdot 5/3} = 44\sqrt{3} = 76.21 \text{ A}$$

$$P = \sqrt{3} V_e I_e \cos \varphi = 17.4 \text{ kW}$$

$$Q = \sqrt{3} V_e I_e \sin \varphi = 23.2 \text{ kVAR}$$

TRIFASE 1

8)

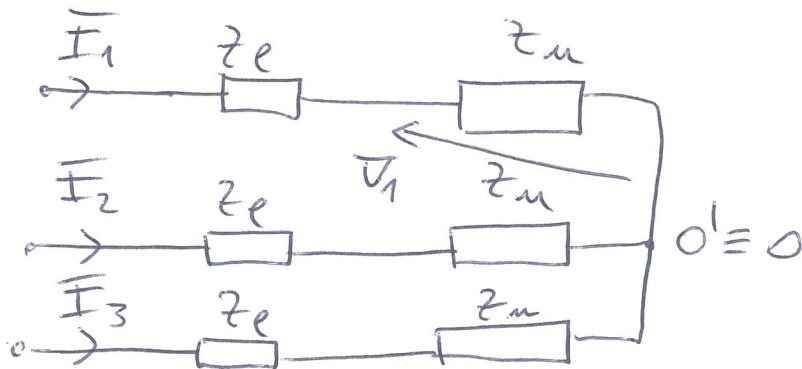

$$z_n = 3 + 4j \Omega$$

$$|z_n| = 5 \Omega$$

$$z_e = 0.1 + 0.2j \Omega$$

$$\varphi_n = 0.927 \text{ rad}$$

220 V 3 ϕ

$$z_T = 3.1 + 4.2j \Omega = 5.22 e^{j0.935} \Omega$$

$$I_e = \frac{220}{\sqrt{3}} \frac{1}{|z_T|} = 24.33 \text{ A}$$

$$|\bar{V}_1| = \frac{|z_n|}{|z_n + z_e|} |\bar{E}_1| = \frac{5}{5.22} 127 = 121.6 \text{ V}$$

$$P_n = 3 \times 121.6 \times 24.33 \times \cos 0.927 = 5327 \text{ W}$$

$$Q_n = 3 \times 121.6 \times 24.33 \times \sin 0.927 = 7099 \text{ VAR}$$

$$P_e = 3 R_e I_e^2 = 3 \times 0.1 \times 24.33^2 = 178 \text{ W}$$

$$P_T = 3 \times 127 \times 24.33 \times \cos 0.935 = 5505 \text{ W}$$

$$Q_T = 3 \times 127 \times 24.33 \times \sin 0.935 = 7458 \text{ VAR}$$