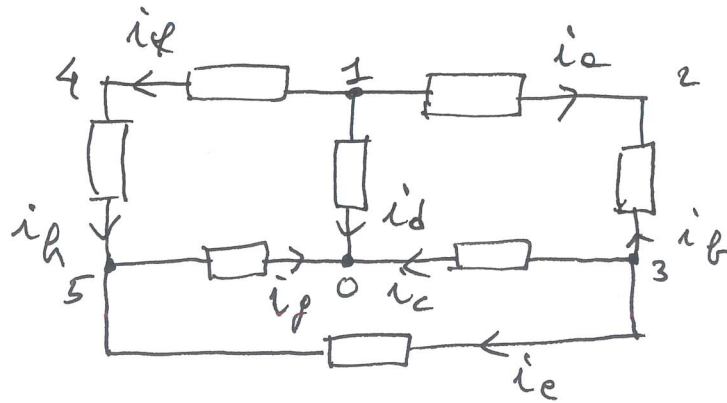


ESERCIZI DA MOODLE


1)



Sapendo che $i_{30} = 3A$ e $i_{10} = 9,3A$
calcolare i_{50} .

$$i_{50} = -(i_{30} + i_{10}) = -12,3 A$$

2)

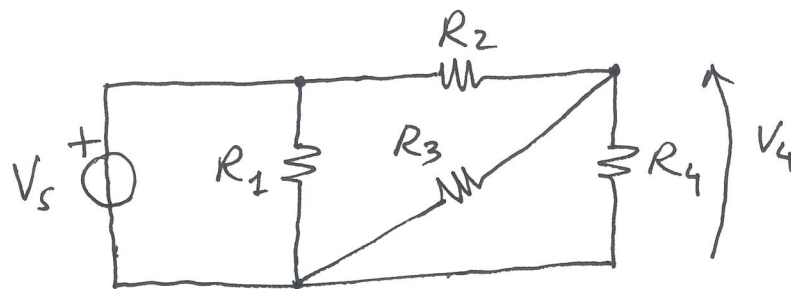


Calcolare V_4 sapendo che :

$$V_s = 12V, R_1 = 15\Omega, R_2 = 3,3\Omega, R_3 = 8,2\Omega, R_4 = 8,2\Omega$$

$$V_4 = \frac{(R_3 || R_4)}{(R_3 || R_4) + R_2} V_s = \frac{4,1}{4,1 + 3,3} 12 = 6,65 V$$

3)

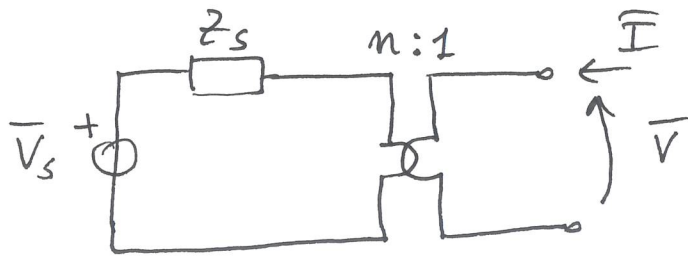

Supponendo che : $\bar{V}_s = 6,9 + 1,1j \text{ V}$, $n = 2$
 $z_s = 12,2 + 1,1j \Omega$


Calcolare $|\bar{I}_{eq}|$ di Norton.

Mettere in corto circuito i terminali del bipolo.
 Nelle equazioni del trasformatore :

$$\bar{I}_1 = -\frac{1}{n} \bar{I}_2 \Rightarrow \bar{I}_{eq} = n \bar{I}_1$$

$$|\bar{I}_1| = \frac{|\bar{V}_s|}{|z_s|} = 0,57 \text{ A} \Rightarrow |\bar{I}_{eq}| = 1,14 \text{ A}$$

4)

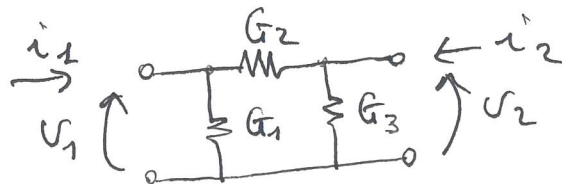


Supponendo che $G_1 = 0,4 \Omega^{-1}$, $G_2 = 0,5 \Omega^{-1}$, $G_3 = 0,3 \Omega^{-1}$
 calcolare R_{21} della matrice delle resistenze.

$$\underline{G} = \begin{bmatrix} 0,9 & -0,5 \\ -0,5 & 0,8 \end{bmatrix} \quad \underline{R} = \underline{G}^{-1}$$

$$R_{21} = \frac{0,5}{\det(\underline{R})} = 1,064 \Omega$$

5)

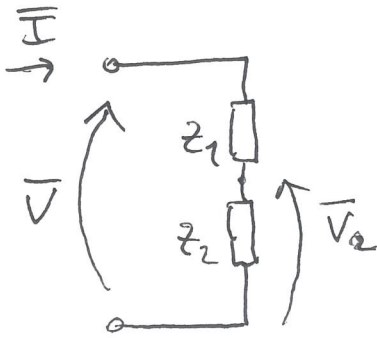

Prendendo che:

$$\bar{V} = 100 \text{ V}$$

$$z_1 = 3 - 5j \ \Omega$$

$$z_2 = 3,8 + 6,8j \ \Omega$$

Calcolare P_2 .


$$P_{C2} = \bar{V}_2 \bar{I}^* = \frac{|\bar{V}_2|^2}{z_2^*}$$

$$P_2 = \text{Re}\{P_{C2}\} = \frac{|\bar{V}_2|^2 R_2}{R_2^2 + X_2^2}$$

$$|\bar{V}_2| = \left| \frac{z_2}{z_1 + z_2} \right| |\bar{V}| = 110,7 \text{ V}$$

$$P_2 = 767,4 \text{ W}$$


6)

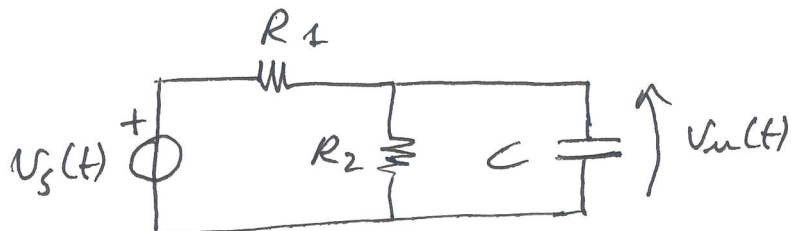Prendendo che: $R_1 = 4175,1 \ \Omega$, $R_2 = 6248,0 \ \Omega$, $C = 6,8 \ \mu\text{F}$ Calcolare il polo della funzione di rete $H(s) = \frac{V_m(s)}{V_5(s)}$

$$H(s) = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + sC} = \frac{R_2}{(R_1 + R_2) + sCR_1R_2}$$

$$p = \frac{-(R_1 + R_2)}{CR_1R_2} = -58,76 \text{ s}^{-1}$$

7)

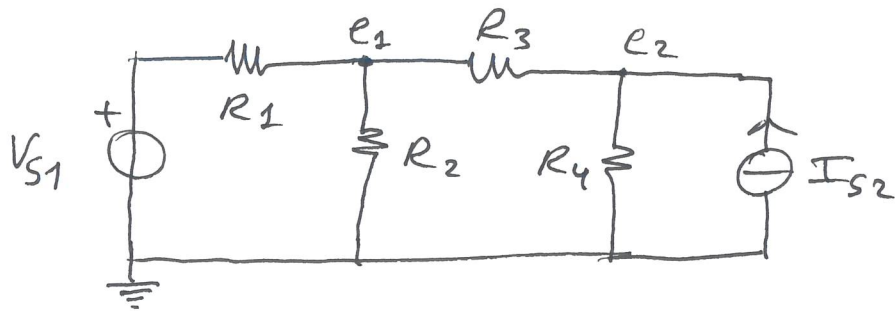


Prevedo che: $V_S = 12V$, $I_{S2} = 3A$, $R_1 = 1,1\Omega$

$$R_2 = 9,50\Omega, R_3 = 2,4\Omega, R_4 = 1,0\Omega$$

Calcolare l'elemento G_{22}^{mod} della matrice modale.

$$\frac{e_2 - e_1}{R_3} + \frac{e_2}{R_4} = I_{S2} \quad G_{22}^{mod} = \frac{1}{R_3} + \frac{1}{R_4} = 1,42\Omega^{-1}$$

8)

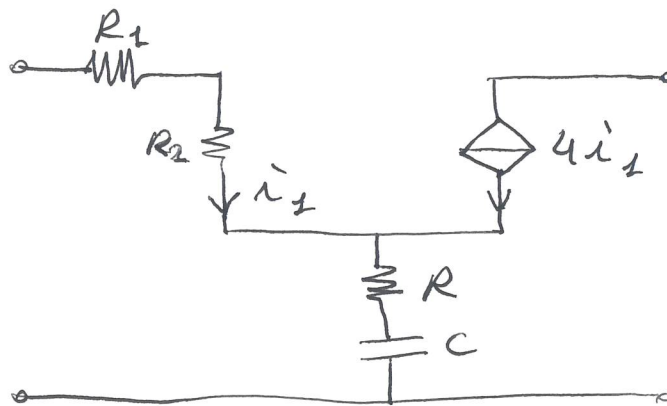


Prevedo che: $R = 6,2\Omega$ e $C = 221,6\mu F$, $\omega = 100\text{rad/s}$

Calcolare il modulo di Z_1 (Miller II)

$$Z_1 = Z(1 + \beta) = 5Z \quad |Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} = 45,55\Omega$$

$$|Z_1| = 5|Z| = 227,75\Omega$$

9)

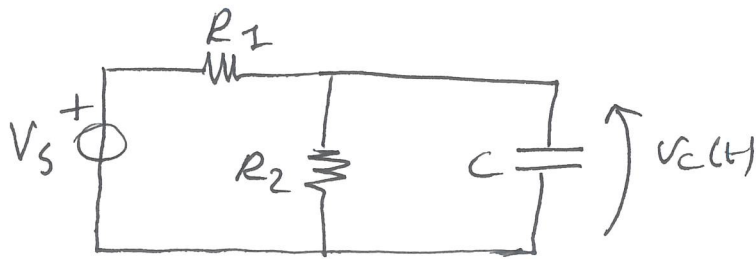

Dato che : $v_C(0) = V_0 = 1V$, $V_s = 12V$, $R_1 = 10\Omega$
 $R_2 = 5,2\Omega$, $C = 1,9mF$


Calcolare $v_C(t)$ per $t = 5ms$

$$v_C(t) = (1 - V_p) e^{-t/\tau_c} + V_p$$

$$V_p = \frac{R_2}{R_1 + R_2} V_s = 4,1V \quad \tau_c = (R_1 || R_2) C = 6,5ms$$

$$v_C(5 \times 10^{-3}) = (1 - 4,1) e^{\frac{-5 \times 10^{-3}}{6,5 \times 10^{-3}}} + 4,1 = 2,67V$$

10)

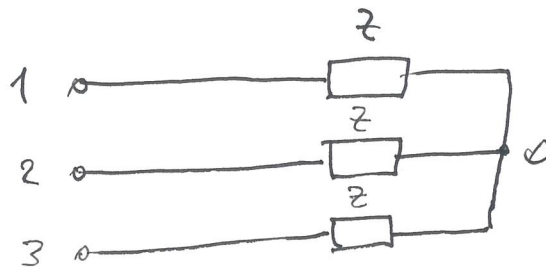

Dato che : $V_e = 400V$, $Z = 41,4 + j3,9\Omega$

Calcolare Q_u .

$$I_e = \frac{400}{\sqrt{3}} \frac{1}{|Z|} = 5,55A$$

$$Q = \sqrt{3} V_e I_e \sin\varphi = 360,6 VAR$$