

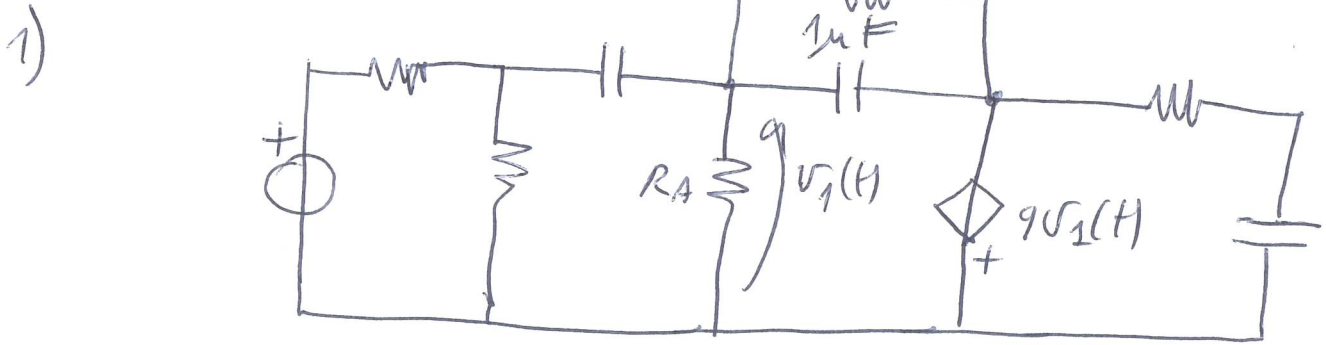


MILLER

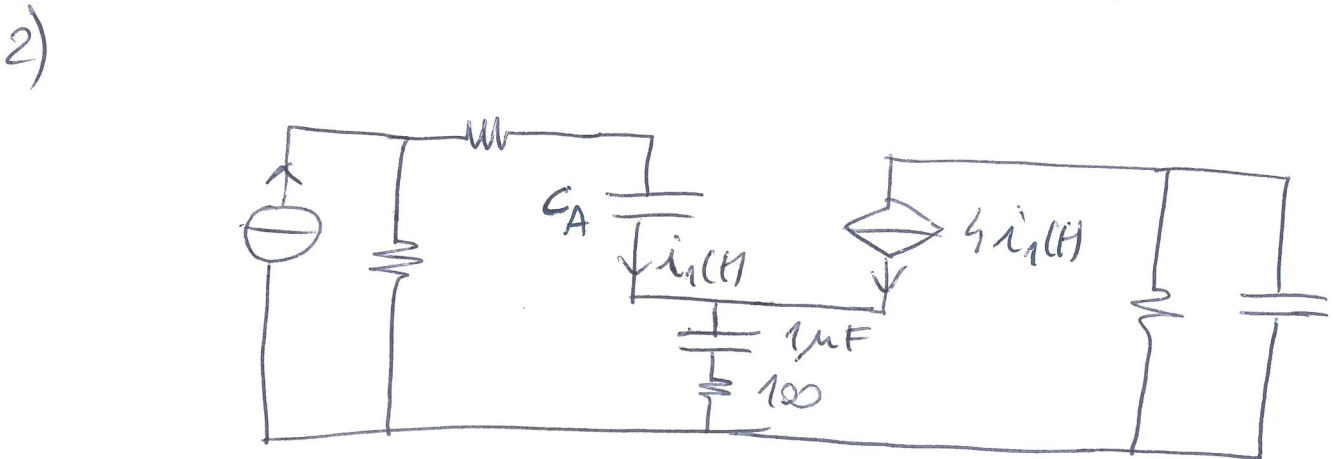

$$R_1 = \frac{1000}{1 - (-9)} = 100 \Omega$$

$$C_1 = 10^{-6} [1 - (-9)] = 10^{-5} F$$

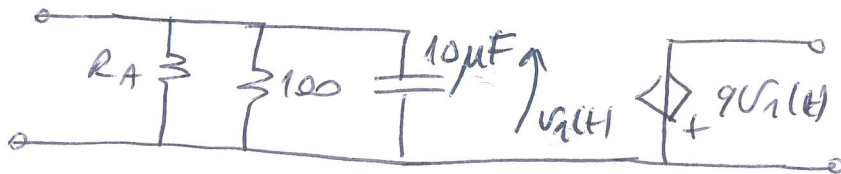

$$R_1 = 100 (1 + 4) = 500 \Omega$$

$$C_1 = 10^{-6} / (1 + 4) = 0.2 \mu F$$

