



UNIVERSITÀ
DEGLI STUDI DI TRIESTE




Combinational circuits

A.Carini – Digital Integrated Circuits


Combinational circuits

- Implement the following functions:
 - Numerical operations
 - Data addressing and selection
 - Coders and decodes
 - Multiplexers and demultiplexers
 - Implementation of generic logic functions
 - Logic elements
 - Programmable logic arrays


Matrix structure

 


Bit-slice

 


Input and output buffer stages

 


Adders and subtractors

 


Comparators

 

Comparators

 

Decoders

 


Decoders

Tabella 10.1 Tabella della verità per un decodificatore da 2 bit.

Ingressi			Uscite			
En	A_0	A_1	Y_0	Y_1	Y_2	Y_3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1


Decoders

 


Decoders

$$\begin{aligned} Y_0 &= \overline{A_0} \cdot \overline{A_1} = \overline{A_0 + A_1} \\ Y_1 &= A_0 \cdot \overline{A_1} = \overline{\overline{A_0} + A_1} \\ Y_2 &= \overline{A_0} \cdot A_1 = \overline{A_0 + \overline{A_1}} \\ Y_3 &= A_0 \cdot A_1 = \overline{\overline{A_0} + \overline{A_1}} \end{aligned}$$


Decoders

 


Decoders

 


Decoders

 

Decoders

 

Encoders

 

Encoders

Tabella 10.2 Tabella della verità per il codificatore 8-3.


Ingressi								Uscite		
A_0	A_1	A_2	A_3	A_4	A_5	A_6	A_7	Y_0	Y_1	Y_2
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	1	0	0	0	0	0	1
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	0	1	1
0	0	0	0	0	0	0	1	1	1	1

Encoders


$$Y_0 = A_1 + A_3 + A_5 + A_7$$

$$Y_1 = A_2 + A_3 + A_6 + A_7$$


$$Y_2 = A_4 + A_5 + A_6 + A_7$$

 


Encoders

 


Encoders

 


Demultiplexer

 


Demultiplexer

 

Multiplexer

 

Multiplexer

 


Logic element


Tabella 10.3 Funzioni logiche implementabili nell'Unità Logica Booleana.

Y	P_1	P_2	P_3	P_4
OR (A, B)	1	1	1	0
NOR (A, B)	0	0	0	1
AND (A, B)	1	0	0	0
NAND (A, B)	0	1	1	1
XOR (A, B)	0	1	1	0
XNOR (A, B)	1	0	0	1


Logic element

 


Programmable logic array (PLA)

 


Programmable logic array (PLA)

 

Programmable logic array (PLA)

 

Programmable logic array (PLA)

 

Vedere:

- Paolo Spirito, “Elettronica Digitale”, Ed. McGraw-Hill
 - Cap. 10.09-10.10