
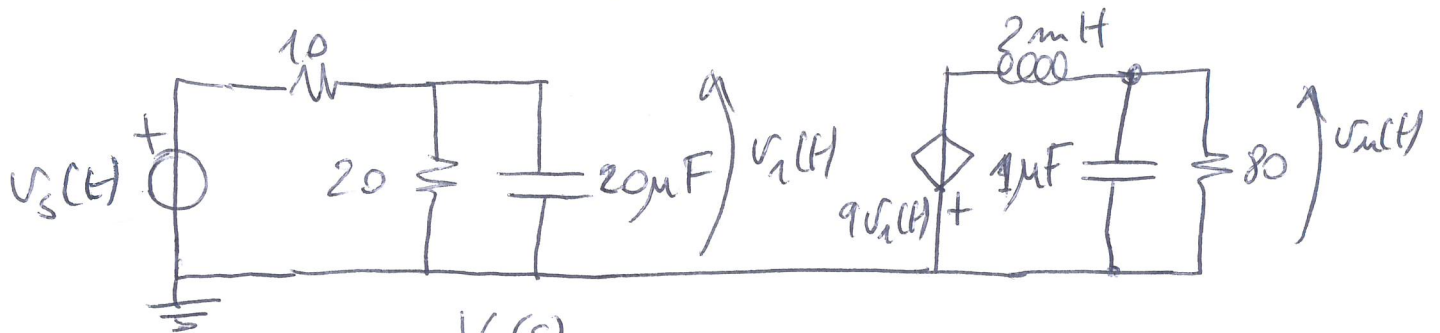


FUNZIONI DI RETE

1) a)

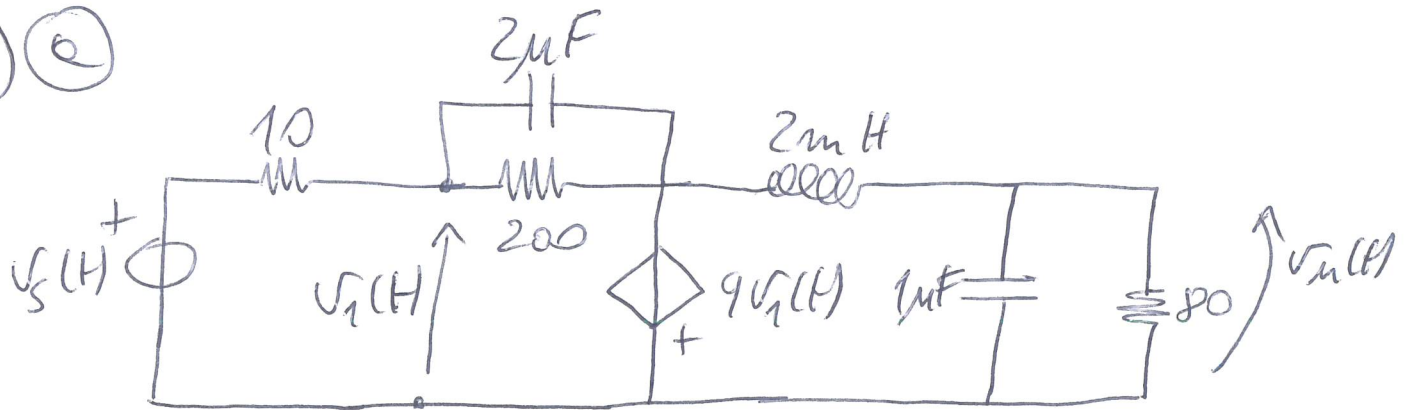

$$V_1(s) = \frac{\frac{V_s(s)}{10}}{\frac{1}{10} + \frac{1}{20} + sC_1} = \frac{2}{3} \frac{V_s(s)}{1 + sC_1 \frac{20}{3}}$$

$$V_u(s) = \frac{\frac{-9V_1(s)}{sL}}{\frac{1}{sL} + \frac{1}{80} + sC_2} = \frac{-9V_1(s) \cdot 80}{80 + sL + s^2 80C_2 L}$$

$$V_u(s) = \frac{-9 V_1(s)}{1 + s \frac{L}{80} + s^2 L C_2}$$

$$H(s) = \frac{V_u(s)}{V_s(s)} = \frac{V_u(s)}{V_1(s)} \cdot \frac{V_1(s)}{V_s(s)}$$

FUNZIONI DI RETE

1) (e)

$$H(s) = -9 \frac{2}{3} \frac{1}{1 + sC_1 \frac{20}{3}} \frac{1}{1 + s \frac{L}{80} + s^2 L_2 C}$$

$$H(s) = -6 \frac{1}{1 + s \frac{4}{3} 10^{-4}} \frac{1}{1 + s \frac{10^{-4}}{4} + s^2 2 \times 10^{-9}}$$

$$H(0) = -6$$

$$\lim_{|s| \rightarrow +\infty} |H(s)| = 0$$

$$\begin{cases} m = 3 \\ n = 0 \end{cases}$$

{ 3 ZERI ∞

$$p_1 = -7500$$

$$p_{2,3} = -6250 \pm j 1250 \sqrt{295}$$

$$\begin{cases} \omega_0^2 = 5 \times 10^8 \\ \omega_0 q = 4 \times 10^4 \end{cases}$$

$$\omega_0 = \sqrt{5} \times 10^4 \text{ rad/s}$$


$$q = \frac{4 \times 10^4}{\sqrt{5} \times 10^4} = \frac{4}{\sqrt{5}} = 1.79$$

CIRCUITO STABILE

$$H(j\omega) = -6 \frac{1}{1 + j\omega \frac{4}{3} \times 10^{-4}} \frac{1}{1 + j\omega \frac{10^{-4}}{4} + (j\omega)^2 2 \times 10^{-9}}$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

$$|H(j0)| = -6$$

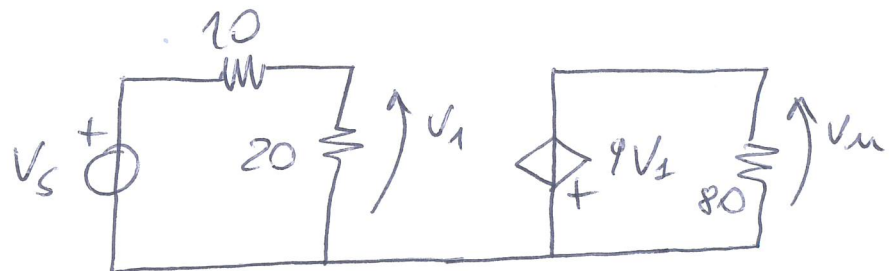

(DC)

FUNZIONI DI RETE



1) ©

DIAGRAMMI DI BODE

$$K_{dB} = 20 \log 6 = 15.56 \text{ dB}$$



$$\log |P_1| = 3.87$$
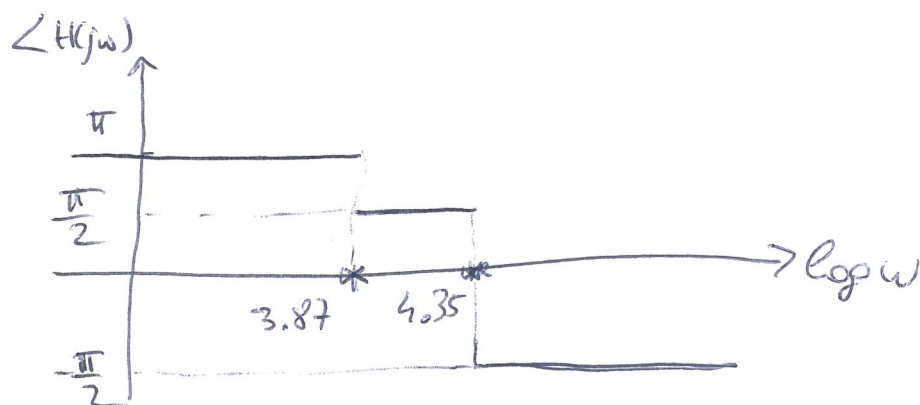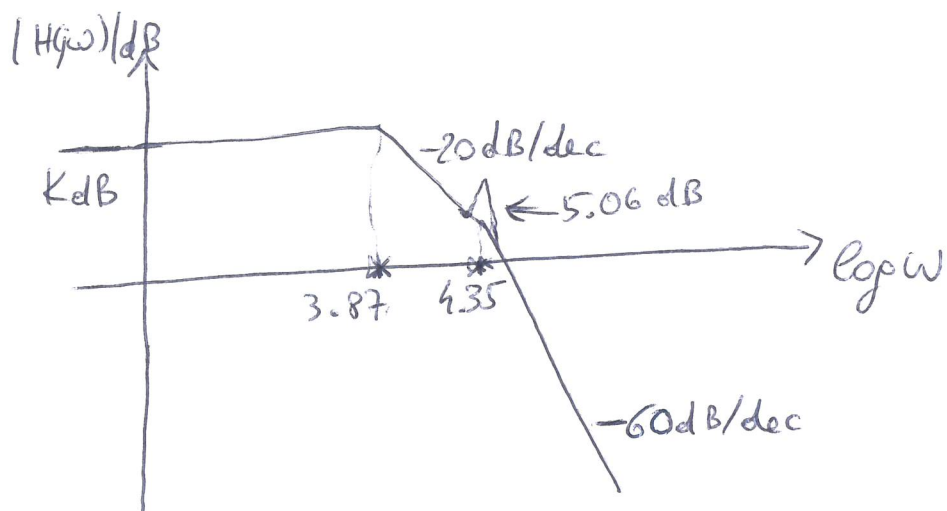
$$\log \omega_0 = 4.35 \quad 20 \log q = 5.06 \text{ dB}$$



FUNZIONI DI RETE

2) @

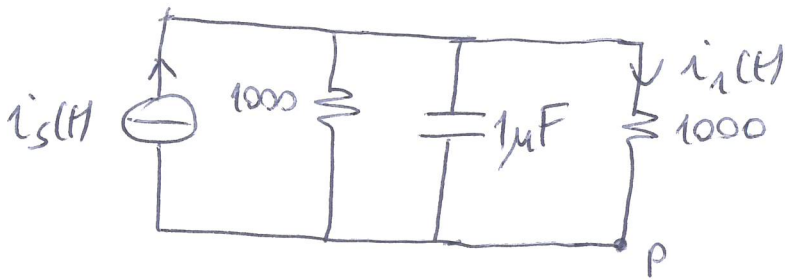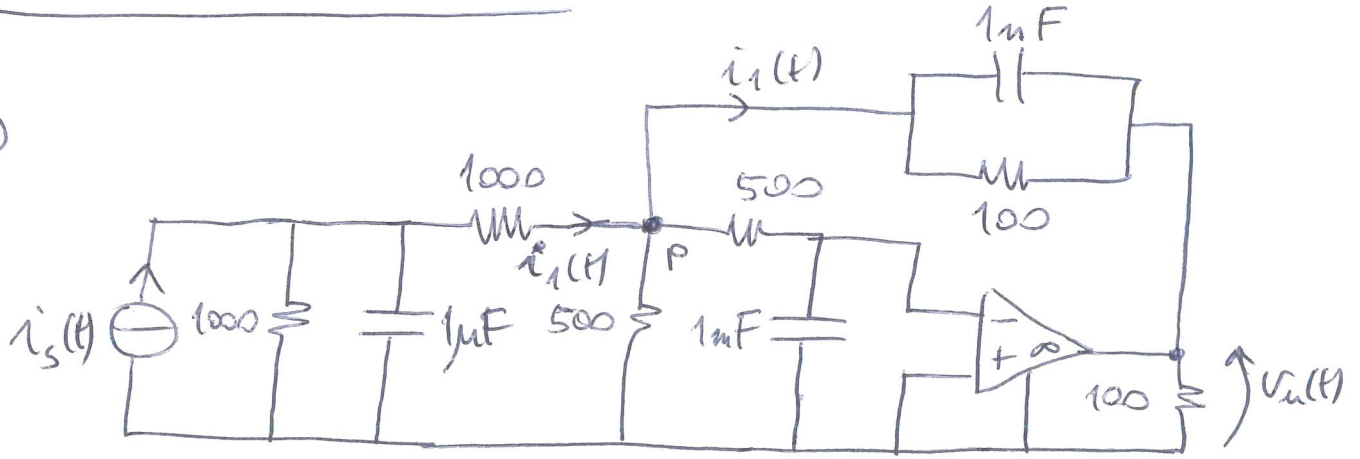

$V_p = 0 \text{ V}$
(MASSA VIRTUALE)

$$I_1(s) = \frac{\frac{1}{1000}}{\frac{1}{1000} + sC_1 + \frac{1}{1000}} \quad I_s(s) =$$

$$= \frac{1}{2 + sC_1 1000} I_s(s) = \frac{1}{2} \frac{1}{1 + sC_1 500} I_s(s)$$

$$V_u(s) = - I_1(s) Z_p(s)$$

$$Z_p(s) = \frac{100}{1 + sC_2 100}$$

$$H(s) = \frac{V_u(s)}{I_s(s)} = \frac{V_u(s)}{I_1(s)} \cdot \frac{I_1(s)}{I_s(s)} = -50 \frac{1}{1 + sC_1 500} \frac{1}{1 + sC_2 100}$$

$$H(s) = -50 \frac{1}{1 + s 5 \times 10^{-4}} \frac{1}{1 + s 10^{-7}}$$

($n=2, m=0$)

FUNZIONI DI RETE

2) (P)

$$H(0) = -50$$


$$\lim_{|s| \rightarrow \infty} |H(s)| = 0$$

2 POLI, 2 ZERI ∞

$$p_1 = -\frac{1}{5} 10^4 = -2000$$

$$p_2 = -\frac{1}{10^7} = -10^{-7}$$

CIRCUITO
STABILE

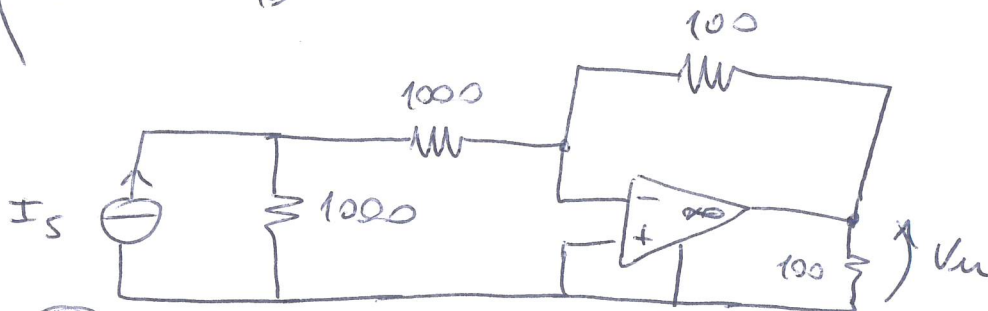

(DC)


$$\frac{V_u}{1000 I_s} = \frac{-100}{2000} \Rightarrow \frac{V_u}{I_s} = -50$$

$$H(j\omega) = -50 \frac{1}{1 + j\omega 5 \times 10^{-4}} \frac{1}{1 + j\omega 10^{-7}}$$

$$20 \log |K| = K_{dB} = 33.98 \text{ dB}$$




$$\log |p_1| = 3.3$$

$$\log |p_2| = 7$$

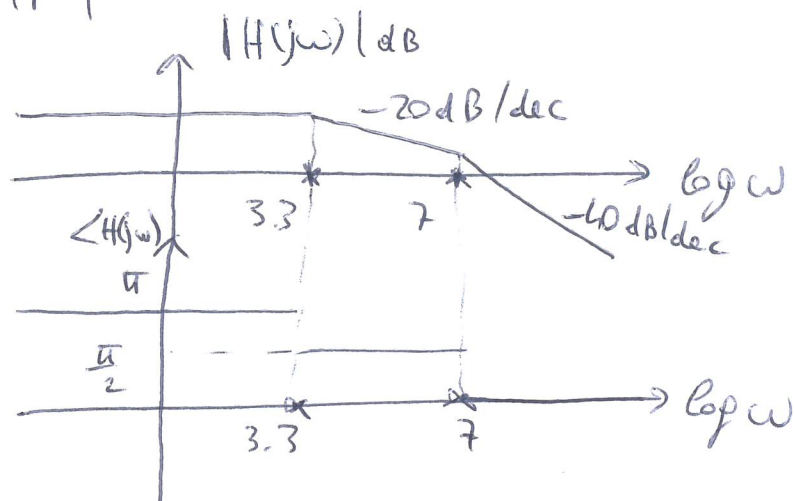

FUNZIONI DI RETE

4) c)

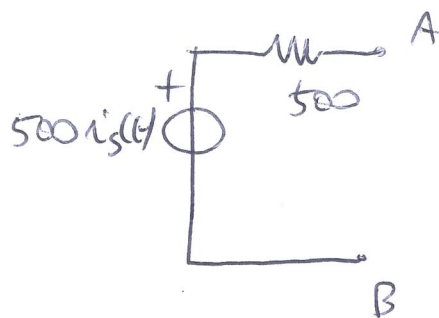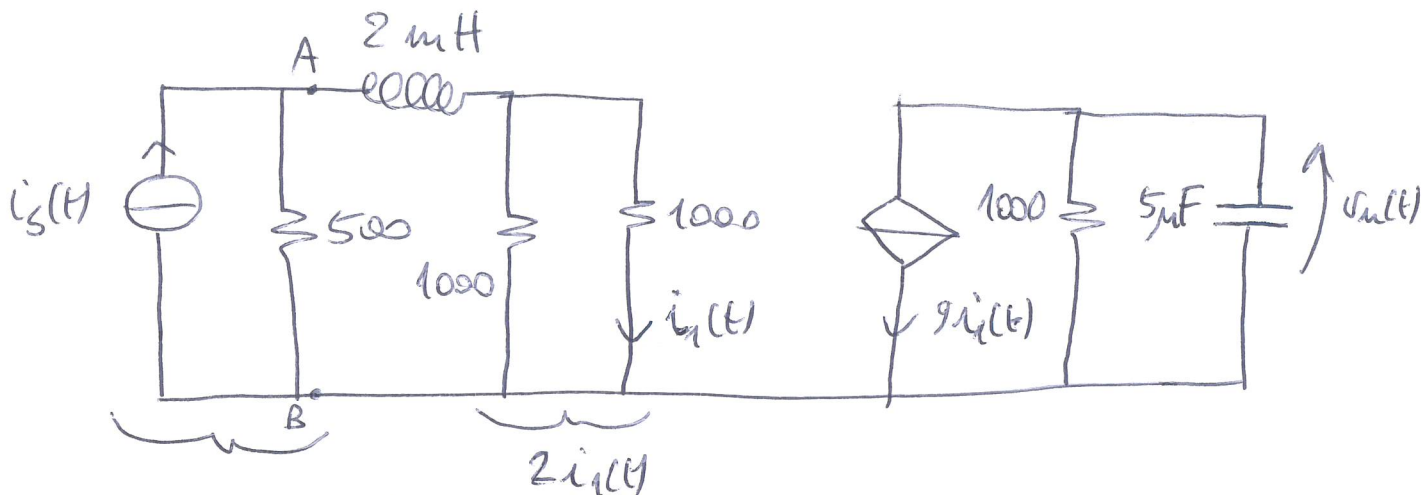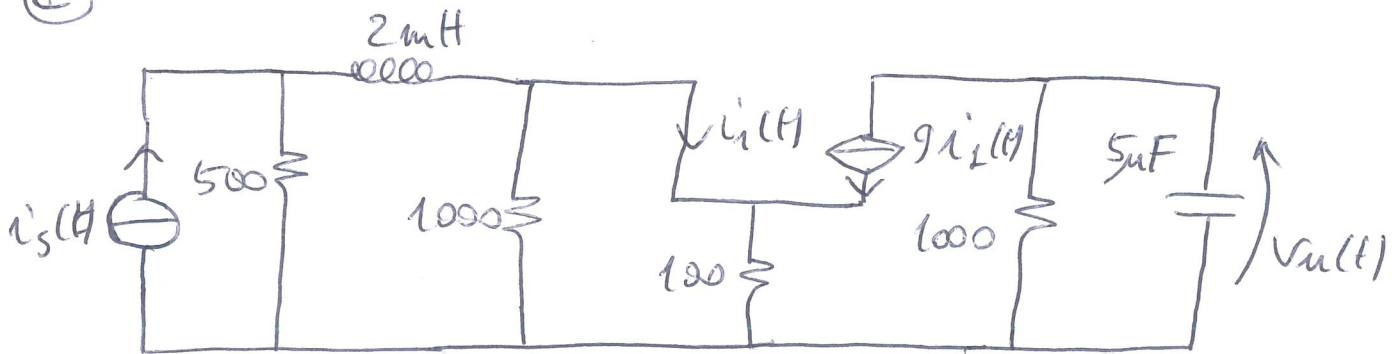

$$F_1(s) = \frac{1}{2} \cdot \frac{500 I_s(s)}{1000 + sL} =$$

$$= \frac{1}{4} \frac{1}{1 + sL/1000} I_s(s)$$

$$V_u(s) = - \frac{1000}{1 + sC1000} 9 F_1(s)$$

$$H(s) = \frac{V_u(s)}{I_s(s)} = -2250 \frac{1}{(1 + sL/1000)(1 + sC1000)}$$

$$H(s) = -2250 \frac{1}{(1 + s2 \cdot 10^{-6})(1 + s5 \cdot 10^{-3})}$$

$$(m=2, n=0)$$

FUNZIONI DI RETE


4) (e)

$$H(0) = -2250$$

$$\lim_{|s| \rightarrow \infty} |H(s)| = 0$$

$$\left\{ \begin{array}{l} 2 \text{ ZERI } \infty \\ p_1 = -\frac{1}{5 \times 10^{-3}} = -200 \\ p_2 = -\frac{1}{2 \times 10^6} = -5 \times 10^5 \end{array} \right. \quad \begin{array}{l} \text{CIRCUITO} \\ \text{STABILE} \end{array}$$
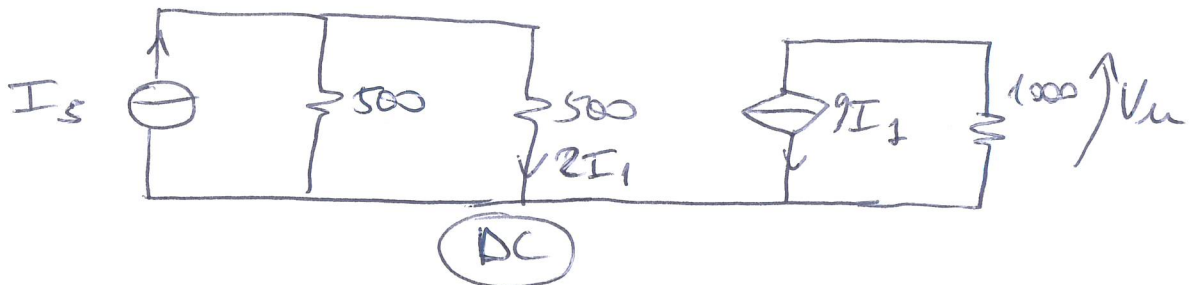
$$H(j\omega) = -2250 \frac{1}{1 + j\omega 2 \times 10^{-6}} \frac{1}{1 + j\omega 5 \times 10^{-3}}$$



$$I_1 = \frac{I_s}{4}$$

$$V_u = -9I_1 \times 1000 = -2250 I_s$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$


$$20 \log |K| = 67 \text{ dB}$$

$$\log |p_1| = 2.3$$

$$\log |p_2| = 5.7$$



FUNZIONI DI RETE

4) (C)

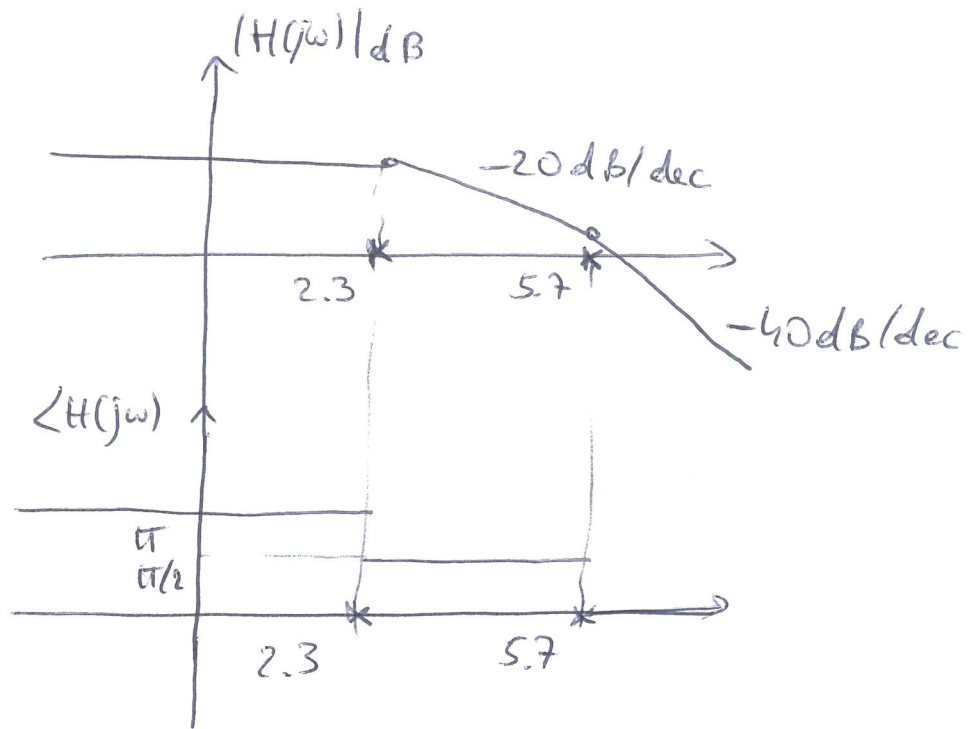

FUNZIONI DI RETE

6) a)

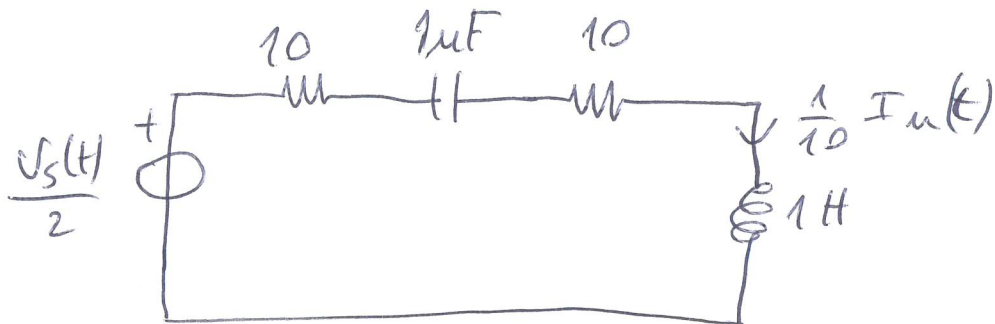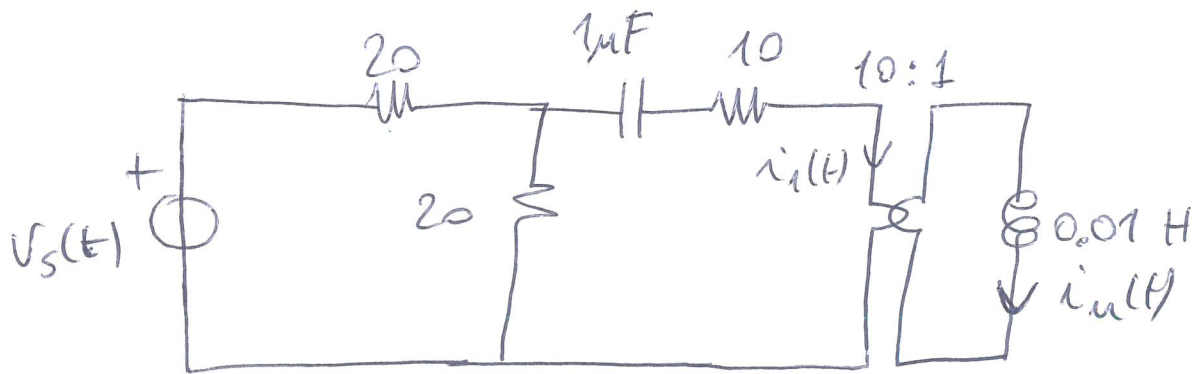

$$Z_1 = n^2 Z_L = n^2 sL = s$$

$$\begin{cases} v_1(t) = n v_2(t) \\ i_1(t) = -\frac{1}{n} i_2(t) = \frac{1}{n} i_u(t) \end{cases}$$

$$\frac{1}{10} I_u(s) = \frac{\frac{V_s(s)}{2}}{20 + \frac{1}{sC} + sL} = \frac{1}{2} \frac{sC}{1 + 20sC + s^2LC} V_s(s)$$

$$H(s) = \frac{I_u(s)}{V_s(s)} = 5C \frac{s}{1 + 20sC + s^2LC}$$

$$H(s) = 5 \times 10^{-6} \frac{s}{1 + s \times 2 \times 10^{-5} + s^2 10^{-6}}$$

$$(M=2, m=1)$$

FUNZIONI DI RETE

6) (P)

$$H(0) = 0$$

$$\lim_{|s| \rightarrow \infty} |H(s)| = 0$$

1 ZERO ORIGINALE

1 ZERO ∞

$$1 p_2 = -10 \pm 1000j$$

CIRCUITO
STABILE

$$\omega_0^2 = 10^6 \quad \omega_0 = 1000 \text{ rad/s}$$

$$q\omega_0 = \frac{1}{2 \times 10^{-5}} \quad q = \frac{10^5}{2} \frac{1}{1000} = 50$$


$$H(j\omega) = 5 \times 10^{-6} \frac{j\omega}{1 + j\omega 2 \times 10^{-5} + (j\omega)^2 10^{-6}}$$

$$H(j0) = 0 \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

$$20 \log K' = K'_{dB} = -106 \text{ dB}$$


$$\log \omega_0 = 3$$

$$20 \log q = 34 \text{ dB}$$

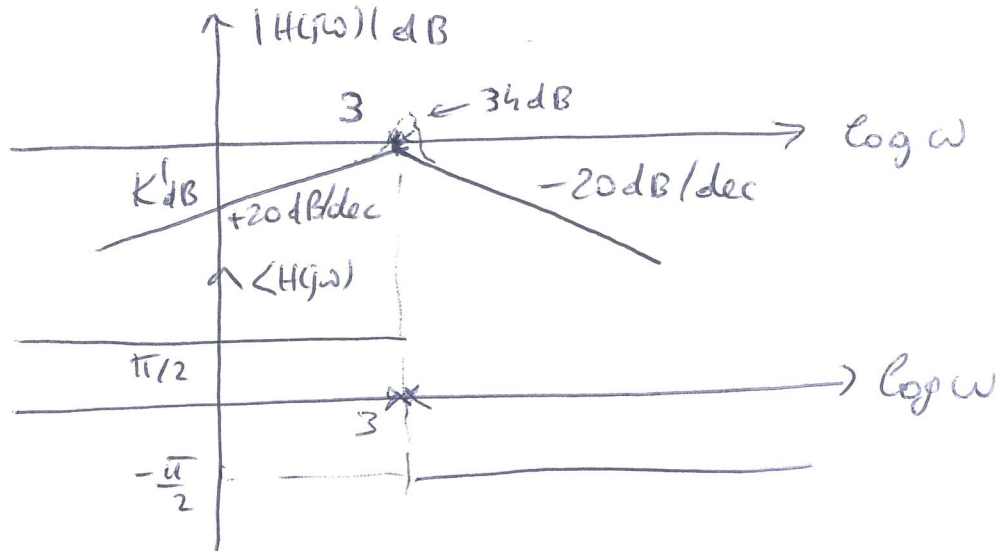

FUNZIONI DI RETE

7) a)

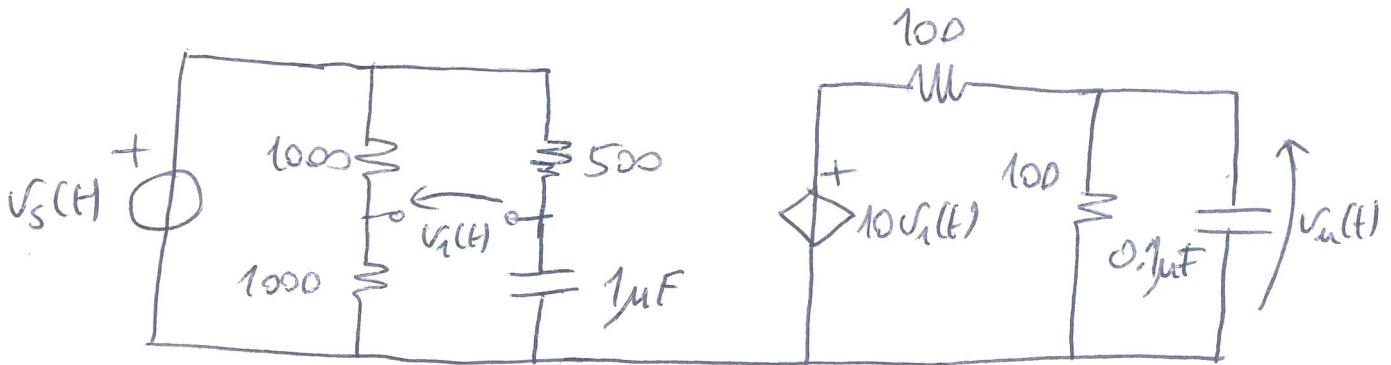

$$V_1(s) = \frac{1000}{1000 + 1000} V_S(s) - \frac{\frac{1}{sC_2}}{\frac{1}{sC_1} + 500} V_S(s)$$

$$\frac{V_1(s)}{V_S(s)} = -\frac{1}{2} \frac{1 - sC_1 500}{1 + sC_1 500} = -\frac{1}{2} \frac{1 - s 5 \times 10^{-4}}{1 + s 5 \times 10^{-4}}$$

$$V_m(s) = \frac{\frac{10V_1(s)}{100}}{\frac{1}{100} + \frac{1}{100} + sC_2} = \frac{5V_1(s)}{1 + sC_2 50}$$

$$= \frac{5V_1(s)}{1 + s 5 \times 10^{-6}}$$

$$H(s) = \frac{V_m(s)}{V_S(s)} = -\frac{5}{2} \frac{1 - s 5 \times 10^{-4}}{1 + s 5 \times 10^{-4}} \frac{1}{1 + s 5 \times 10^{-6}}$$

$$(N=2, m=1)$$

$$\lim_{|s| \rightarrow \infty} |H(s)| = 0 \quad H(0) = -\frac{5}{2}$$


FUNZIONI DI RETE

7) (B)

$$\left\{ \begin{array}{l} 1 \text{ ZERO } \infty \\ z_1 = \frac{1}{5 \times 10^{-4}} = 2000 \\ p_1 = -\frac{1}{5 \times 10^{-4}} = -2000 \\ p_2 = -\frac{1}{5 \times 10^{-6}} = -2 \times 10^5 \end{array} \right. \quad \underline{\text{CIRCUITO STABILE}}$$

$$H(j\omega) = -\frac{5}{2} \frac{1 - j\omega 5 \times 10^{-4}}{1 + j\omega 5 \times 10^{-4}} \frac{1}{1 + j\omega 5 \times 10^{-6}}$$

$$|H(j0)| = -\frac{5}{2} \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

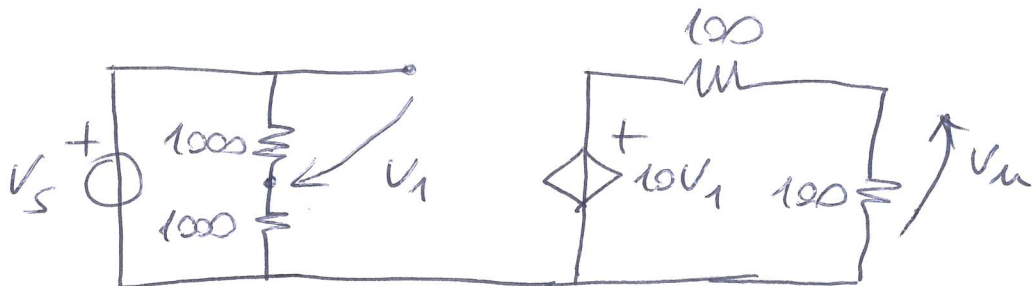

$$V_1 = -\frac{1}{2} V_s \quad V_u = \frac{10 V_1}{2} = -\frac{5}{2} V_s$$

$$K_{dB} = 20 \log |K| = 7.96 \text{ dB}$$


$$\log |z_1| = 3.3$$

$$\log |p_1| = 3.3$$

$$\log |p_2| = 5.3$$



FUNZIONI DI RETE

7) ©

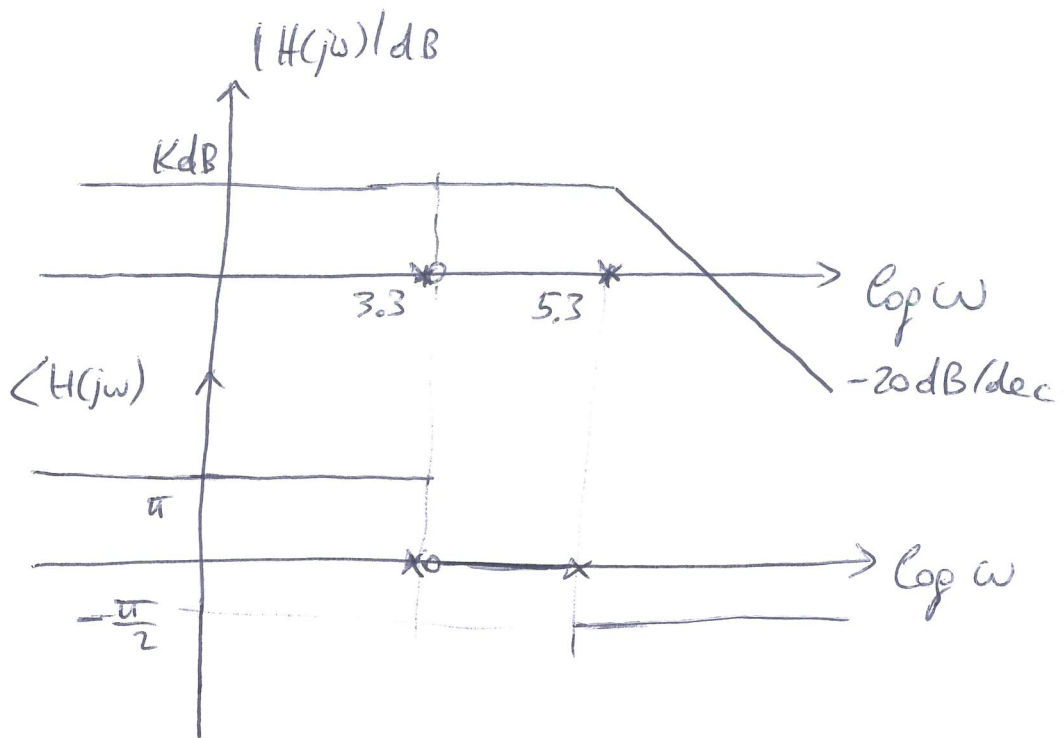

FUNZIONI DI RETE

9) a)

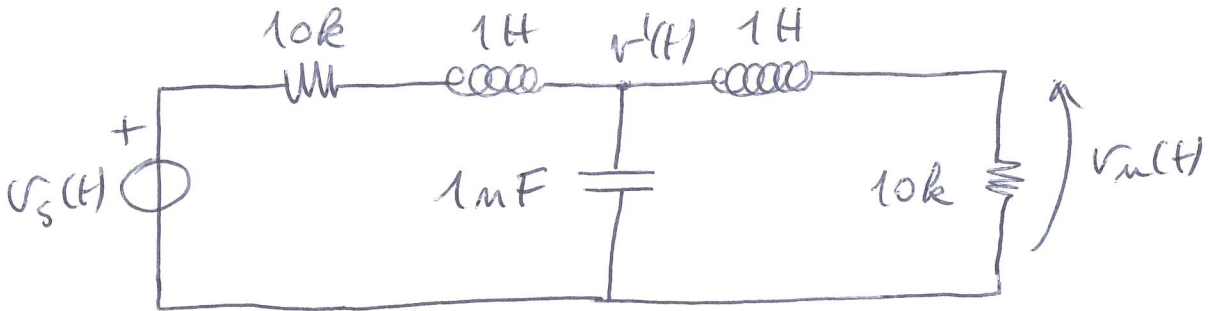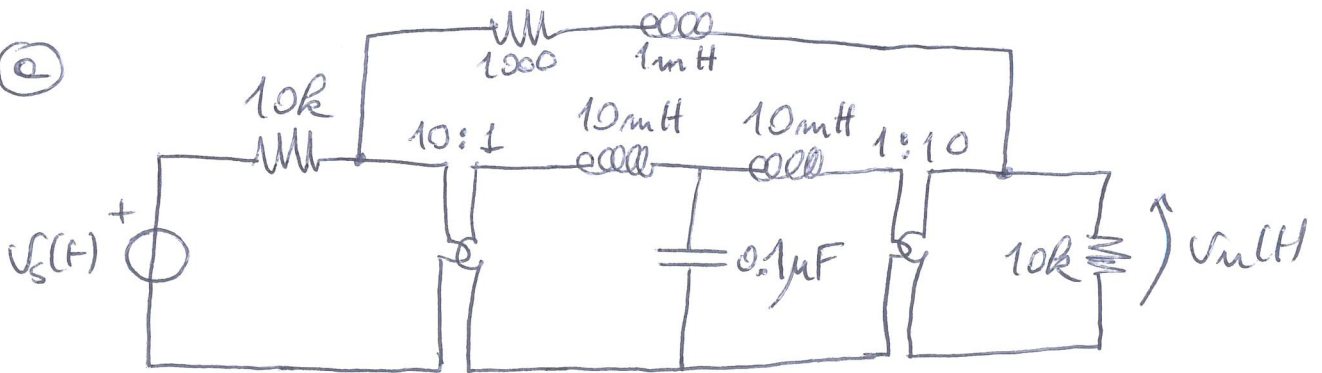

$$V'(s) = \frac{V_s(s)}{10^4 + s} = \frac{1}{10^4 + s} + sC + \frac{1}{10^4 + s} =$$

$$= \frac{V_s(s)}{2 + sC(10^4 + s)} =$$

$$= \frac{V_s(s)}{2 + s \cdot 10^{-5} + s^2 \cdot 10^{-9}}$$

$$V_u(s) = \frac{10^4}{10^4 + s} V'(s) = \frac{1}{1 + s/10^4} V'(s)$$

$$H(s) = \frac{V_u(s)}{V_s(s)} = \frac{1}{2} \frac{1}{1 + s \cdot 10^{-4}} \frac{1}{1 + s \cdot 0.5 \cdot 10^{-5} + s^2 \cdot 0.5 \cdot 10^{-9}}$$

$$(n=3, m=0)$$

$$\begin{cases} H(0) = \frac{1}{2} \\ \lim_{|s| \rightarrow \infty} |H(s)| = 0 \end{cases}$$

FUNZIONI DI RETE


9) (e)

$$\left\{ \begin{array}{l} 3 \text{ ZERI } \infty \\ p_1 = -10^4 \\ p_{23} = -5000 \pm j 44441 \end{array} \right. \quad \text{CIRCUITO STABILE}$$
$$\left\{ \begin{array}{l} \omega_0^2 = 2 \times 10^9 \quad \omega_0 = \sqrt{20} 10^4 \text{ rad/s} \\ q\omega_0 = 2 \times 10^5 \quad q = \sqrt{20} \end{array} \right.$$

$$H(j\omega) = \frac{1}{2} \frac{1}{1 + j\omega 10^{-4}} \frac{1}{1 + j\omega \frac{10^5}{2} + (j\omega)^2 \frac{10^{-9}}{2}}$$

$$|H(j\omega)| = \frac{1}{2}$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

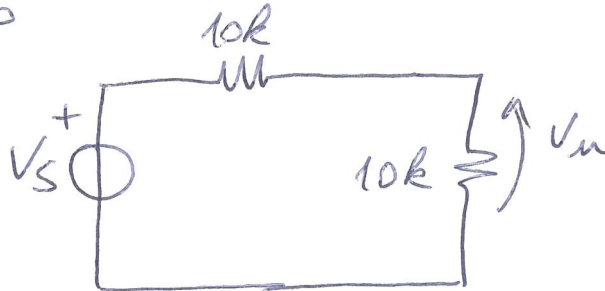

$$V_u = \frac{1}{2} V_S$$

FUNZIONI DI RETE


g) (c)

DIAGRAMMI DI BODE

$$K_{dB} = 20 \log K = -6 \text{ dB}$$



$$\log |k_1| = 4$$
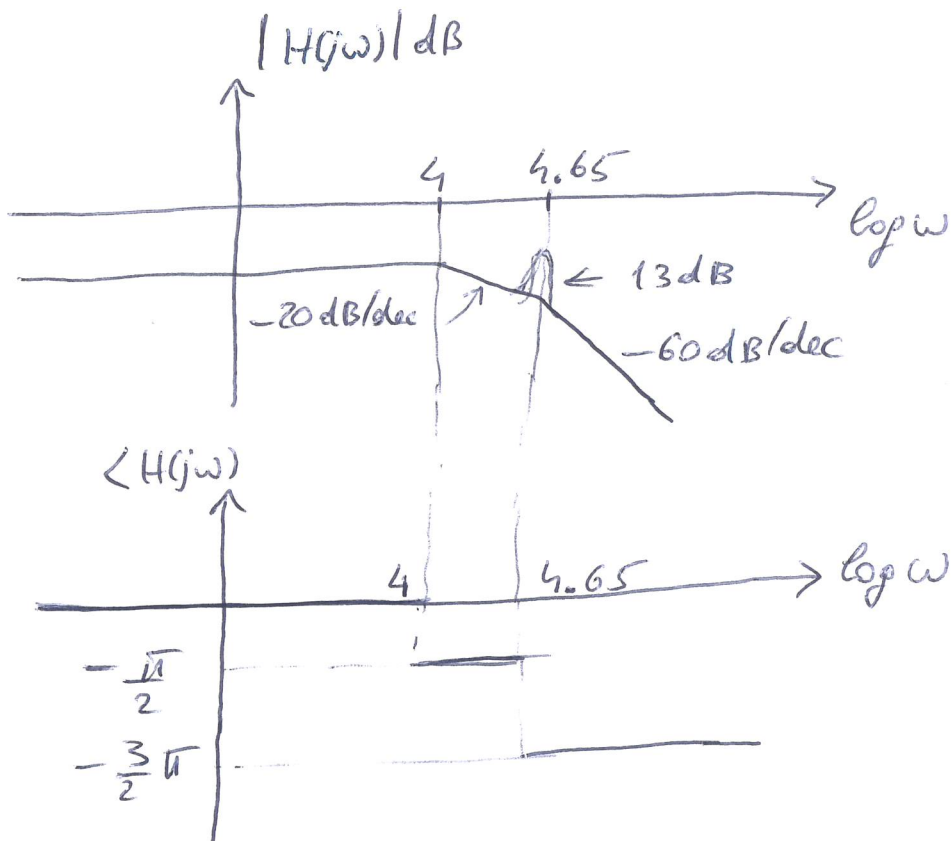
$$\log \omega_0 = 4.65 \quad 20 \log 9 = 13 \text{ dB}$$



FUNZIONI DI RETE

10) e)

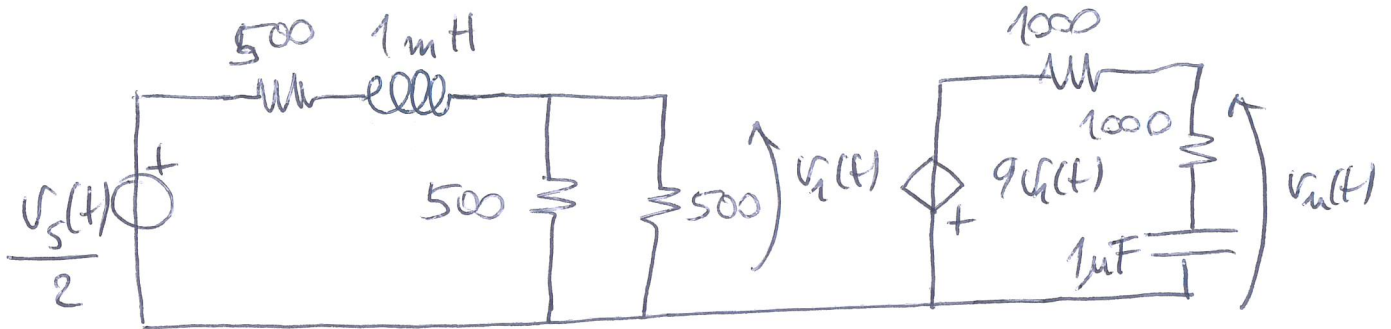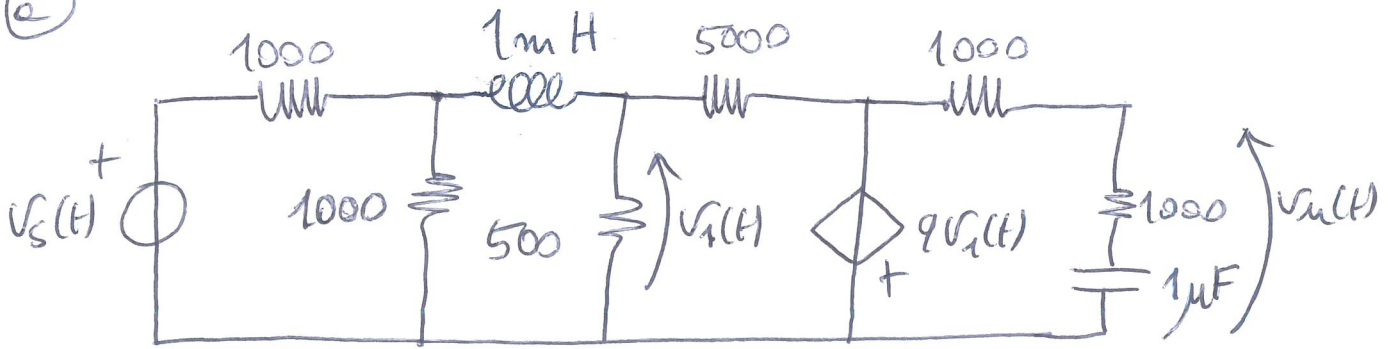

$$V_1(s) = \frac{250}{250 + 500 + sL} \frac{V_S(s)}{2} = \frac{125}{750} \frac{1}{1 + s \frac{L}{750}} V_S(s)$$

$$\frac{V_1(s)}{V_S(s)} = \frac{1}{6} \frac{1}{1 + s \frac{4}{3} \cdot 10^{-6}}$$

$$V_u(s) = \frac{1000 + \frac{1}{sC}}{2000 + \frac{1}{sC}} [-9 V_1(s)] = \frac{1 + sC \cdot 1000}{1 + sC \cdot 2000} (-9) V_1(s)$$

$$\frac{V_u(s)}{V_1(s)} = -9 \frac{1 + s \cdot 10^{-3}}{1 + s \cdot 2 \cdot 10^{-3}}$$

$$H(s) = \frac{V_u(s)}{V_S(s)} = -\frac{3}{2} \frac{1}{1 + s \frac{4}{3} \cdot 10^{-6}} \frac{1 + s \cdot 10^{-3}}{1 + s \cdot 2 \cdot 10^{-3}}$$

$$(M=2, m=1)$$

$$H(0) = -\frac{3}{2} \quad \lim_{|s| \rightarrow \infty} |H(s)| = 0$$

FUNZIONI DI RETE


10) (a)

$$\left\{ \begin{array}{l} 1 \text{ ZERO } \infty \\ z_1 = -\frac{1}{10^{-3}} = -1000 \\ p_1 = -\frac{1}{\frac{4}{3} \cdot 10^{-6}} = -\frac{3}{4} \times 10^6 \\ p_2 = -\frac{1}{2 \times 10^{-3}} = -500 \end{array} \right. \quad \begin{array}{l} \text{CIRCUITO} \\ \text{STABILE} \end{array}$$

$$H(j\omega) = -\frac{3}{2} \frac{1}{1 + j\omega \frac{4}{3} 10^{-6}} \frac{1 + j\omega 10^{-3}}{1 + j\omega 2 \cdot 10^{-3}}$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

$$H(j0) = -\frac{3}{2}$$

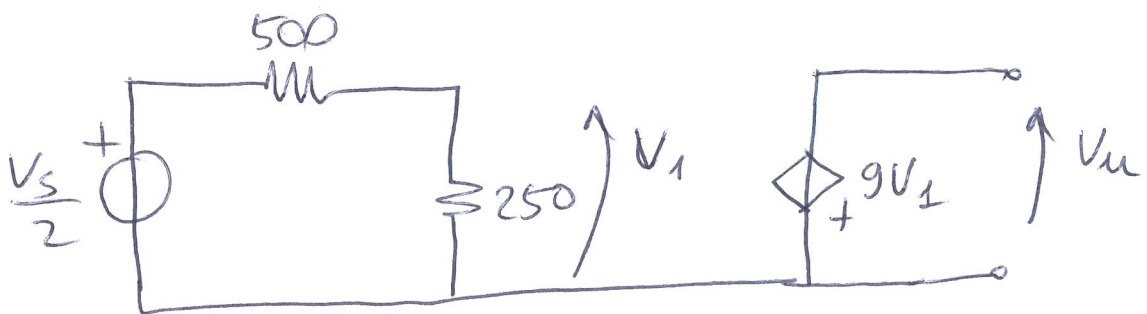

$$V_1 = \frac{250}{250 + 750} \frac{V_s}{2} = \frac{V_s}{6} \quad V_u = -9V_1 = -\frac{3}{2} V_s$$

FUNZIONI DI RETE

10) ©

DIAGRAMMI DI BODE

$$\log |z_1| = 3$$

$$\log |p_1| = 5.875$$

$$\log |p_2| = 2.7$$

$$20 \log |K| = K_{dB} = 3.5$$

