
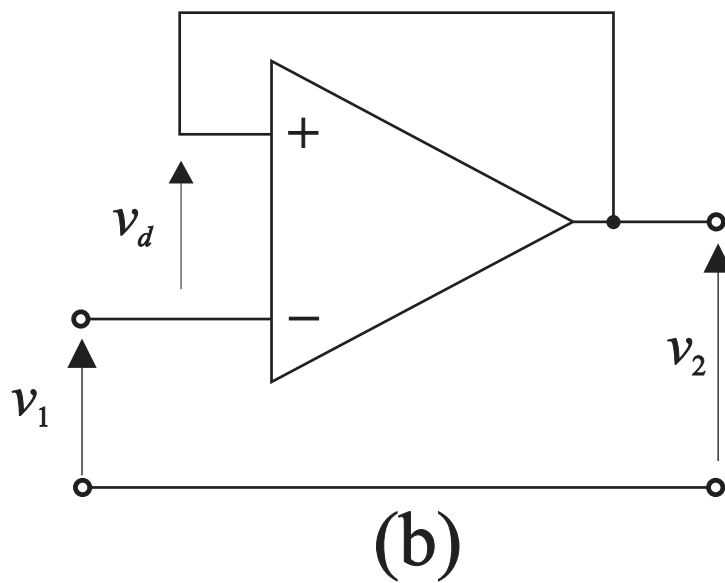


TEORIA dei CIRCUITI



– Voltage follower –

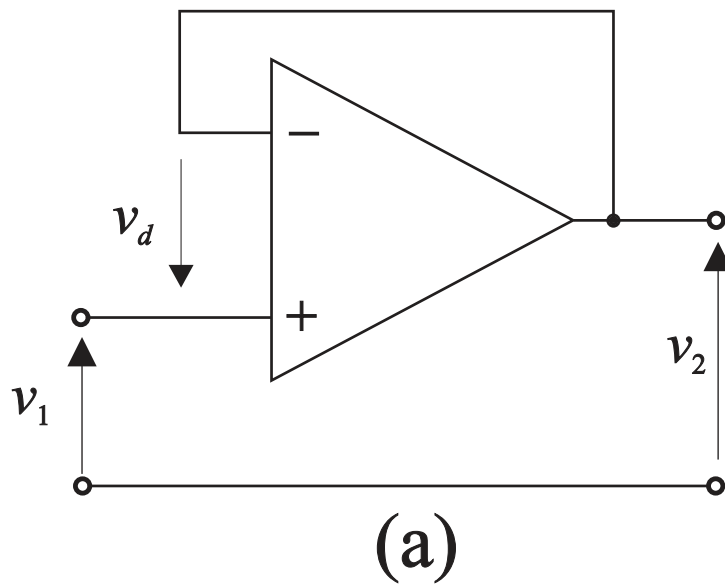

- Due “emitter follower” apparentemente identici. In realtà sono:
 - a) Circuito stabile
 - b) Circuito instabile

- Modelli in zona lineare:

($|v_2| \leq V_{sat}$, $A \gg 1$):

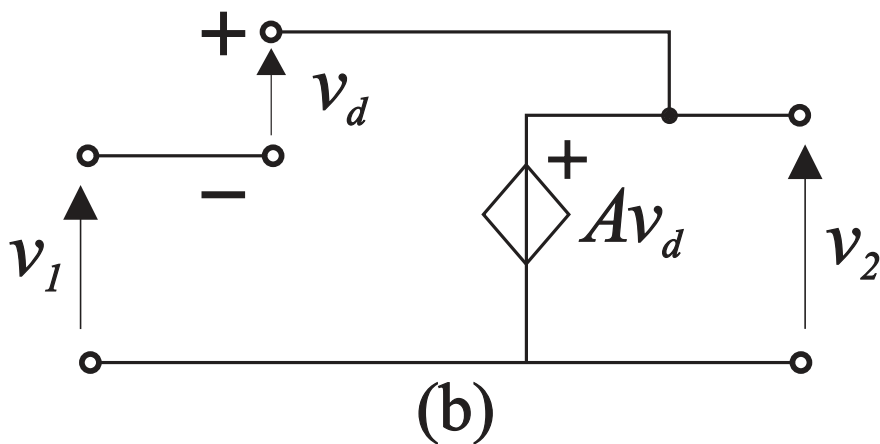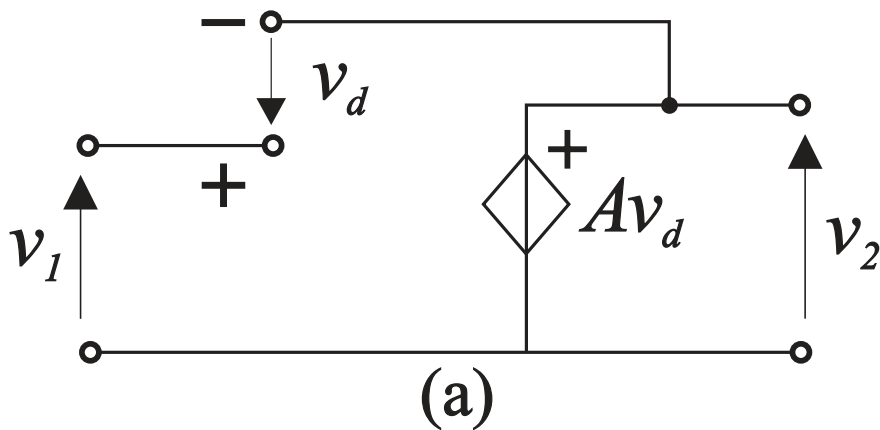

- Equazioni del modello a)

$$\begin{cases} v_d = v_1 - v_2 \\ v_2 = Av_d \end{cases}$$

$$\Rightarrow v_2 = A(v_1 - v_2) \Rightarrow A_v = \frac{v_2}{v_1} = \frac{A}{A+1} < 1$$

$$\lim_{A \rightarrow \infty} A_v = 1 \quad (v_d = 0)$$





- Equazioni del modello b)

$$\begin{cases} v_d = v_2 - v_1 \\ v_2 = Av_d \end{cases}$$

$$\Rightarrow v_2 = A(v_2 - v_1) \Rightarrow A_v = \frac{v_2}{v_1} = \frac{A}{A-1} > 1$$


$$\lim_{A \rightarrow \infty} A_v = 1 \quad (v_d = 0)$$

- Modelli in zona di saturazione:

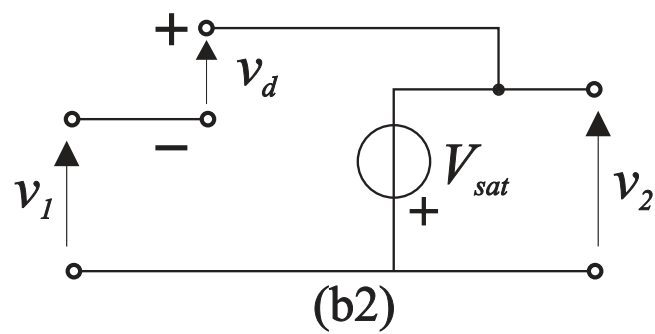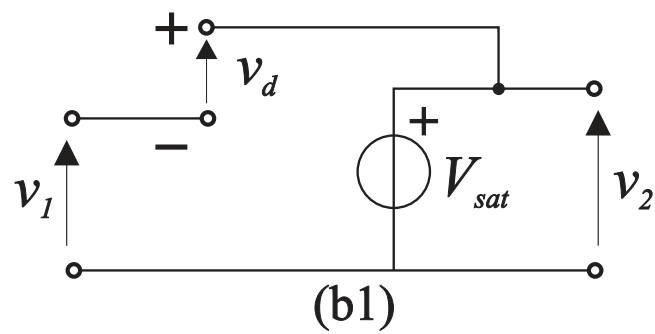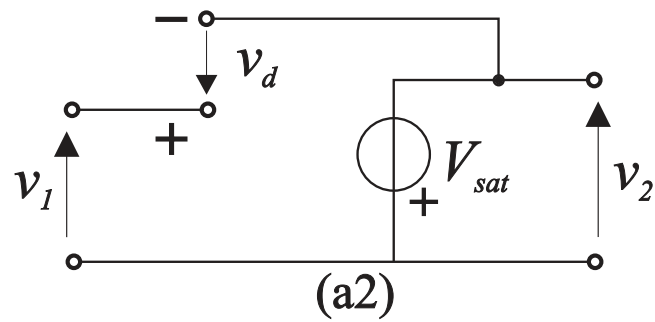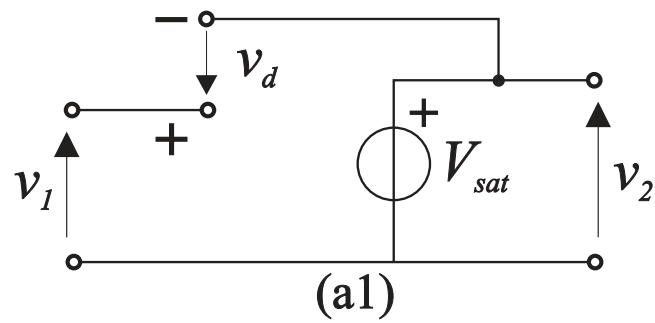


- Equazioni del modello stabile a)
- a1) $v_d = v_1 - v_2 > 0 \Rightarrow v_1 > v_2$
 - $v_1 > V_{sat}$
 - $v_2 = V_{sat}$
- a2) $v_d = v_1 - v_2 < 0 \Rightarrow v_1 < v_2$
 - $v_1 < -V_{sat}$
 - $v_2 = -V_{sat}$
- Equazioni del modello instabile b)
- b1) $v_d = v_2 - v_1 > 0 \Rightarrow v_1 < v_2$
 - $v_1 < V_{sat}$
 - $v_2 = V_{sat}$
- b2) $v_d = v_2 - v_1 < 0 \Rightarrow v_1 > v_2$
 - $v_1 > -V_{sat}$
 - $v_2 = -V_{sat}$

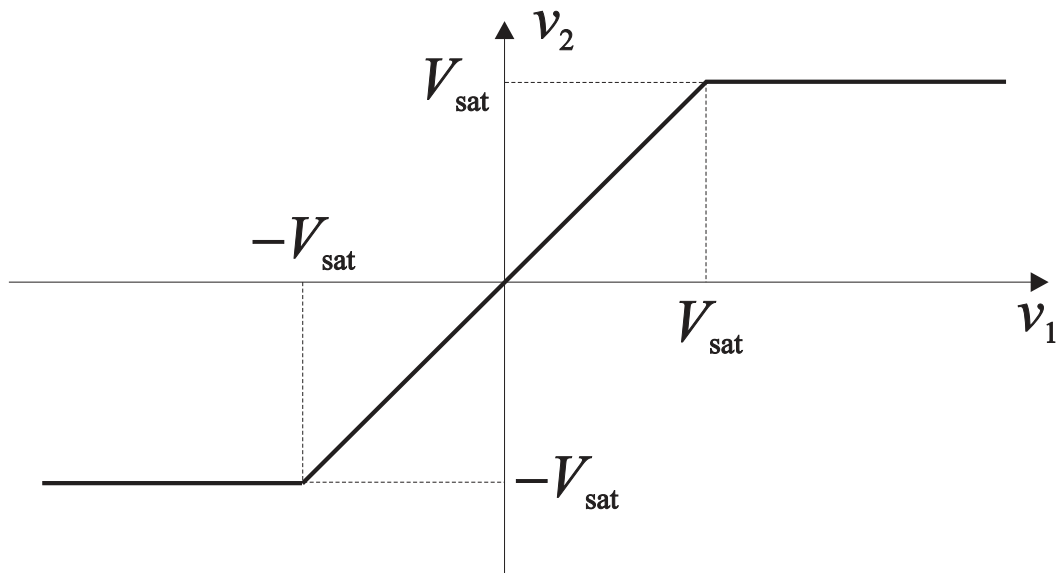- Funzione di rete resistiva dei due modelli:





(a)

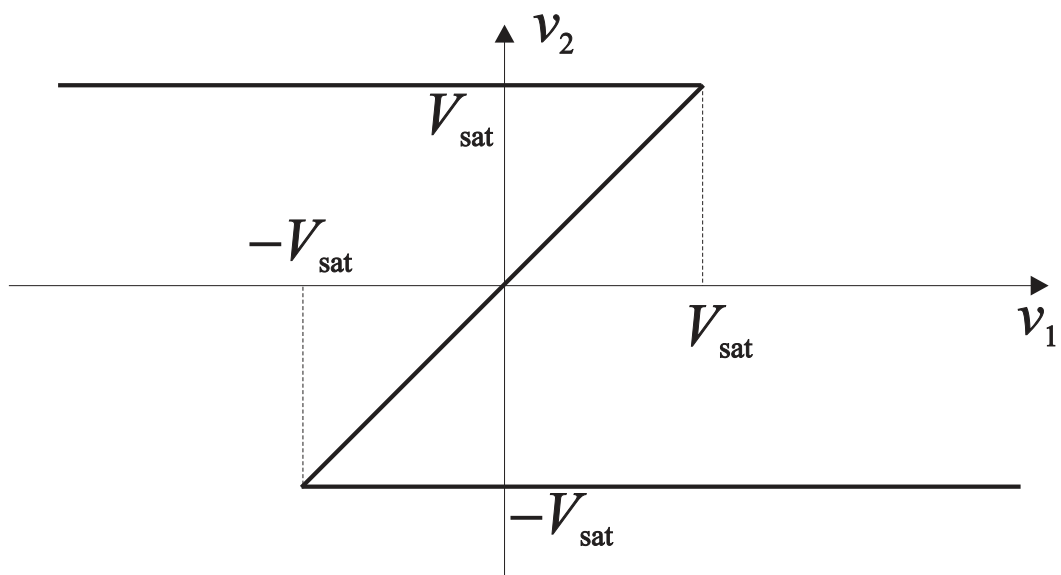

(b)

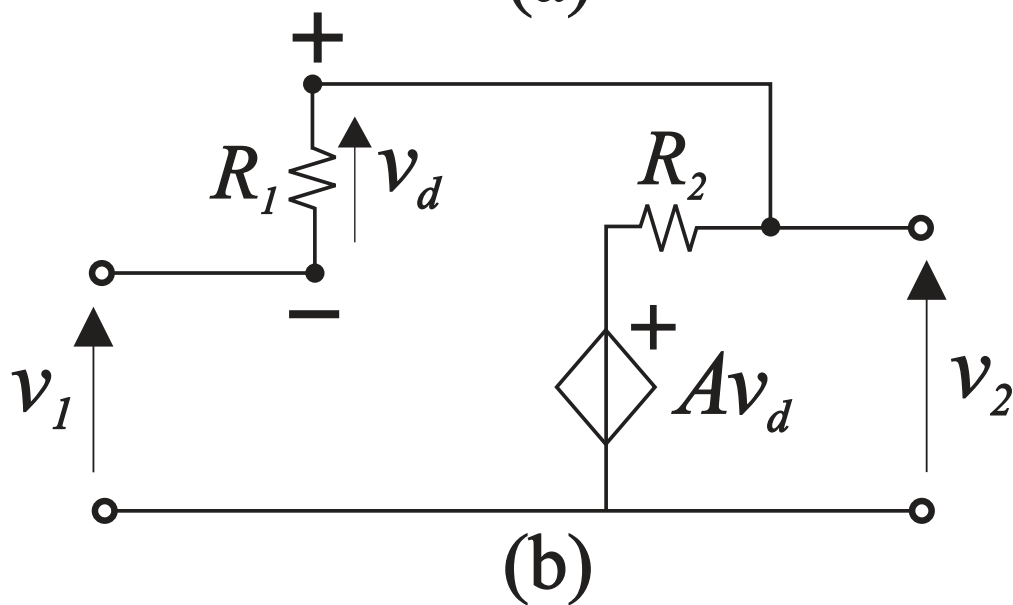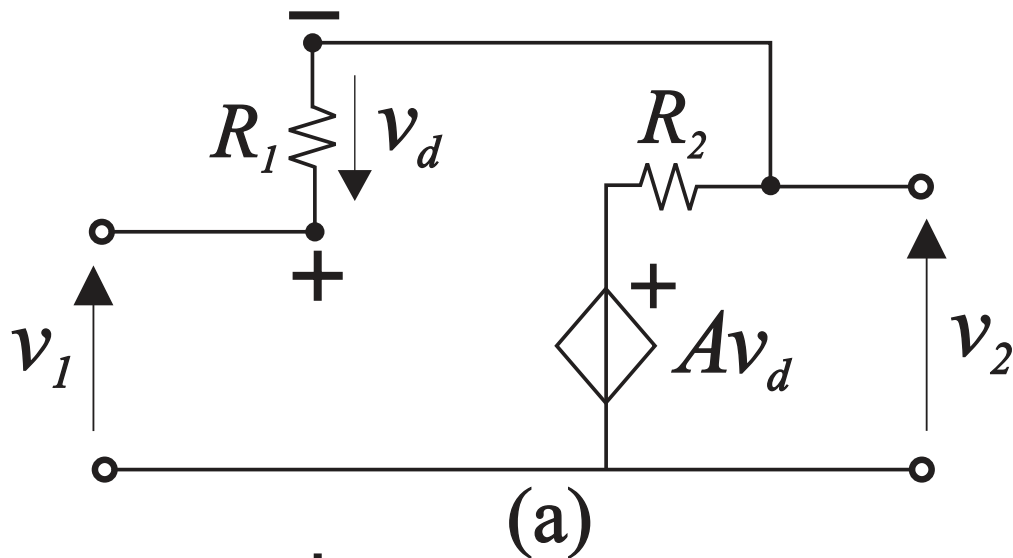- Modelli resistivi con resistenze di ingresso e di uscita: ((a) stabile, (b) instabile)



- Equazioni del modello stabile a)

$$\begin{cases} \frac{v_2 - Av_d}{R_2} + \frac{v_2 - v_1}{R_1} = 0 \\ v_d = v_1 - v_2 \end{cases}$$

$$\frac{v_2 - Av_1 + Av_2}{R_2} + \frac{v_2 - v_1}{R_1} = 0$$

$$A_v = \frac{v_2}{v_1} = \frac{AR_1 + R_2}{(A + 1)R_1 + R_2}$$




- Equazioni del modello instabile b)

$$\begin{cases} \frac{v_2 - Av_d}{R_2} + \frac{v_2 - v_1}{R_1} = 0 \\ v_d = v_2 - v_1 \end{cases}$$

$$\frac{v_2 - Av_2 + Av_1}{R_2} + \frac{v_2 - v_1}{R_1} = 0$$

$$A_v = \frac{v_2}{v_1} = \frac{AR_1 - R_2}{(A - 1)R_1 - R_2}$$

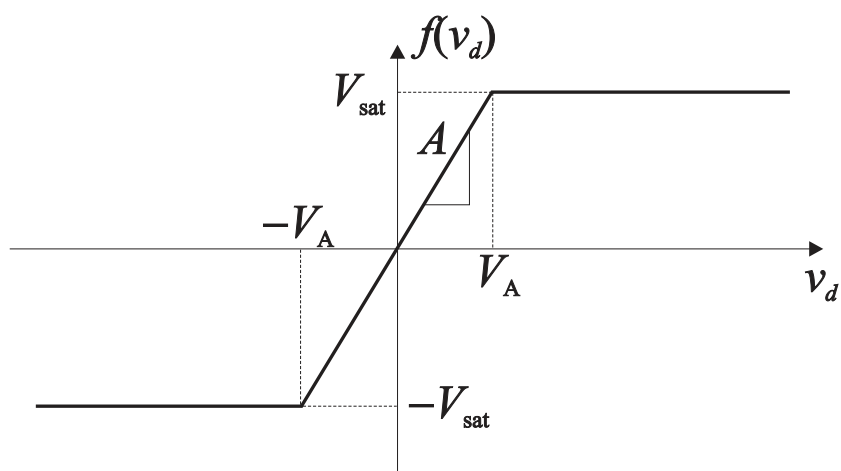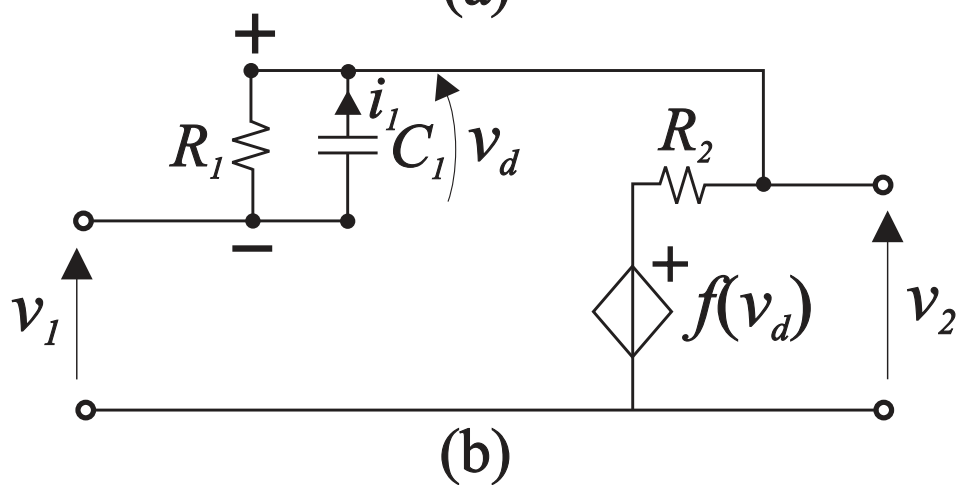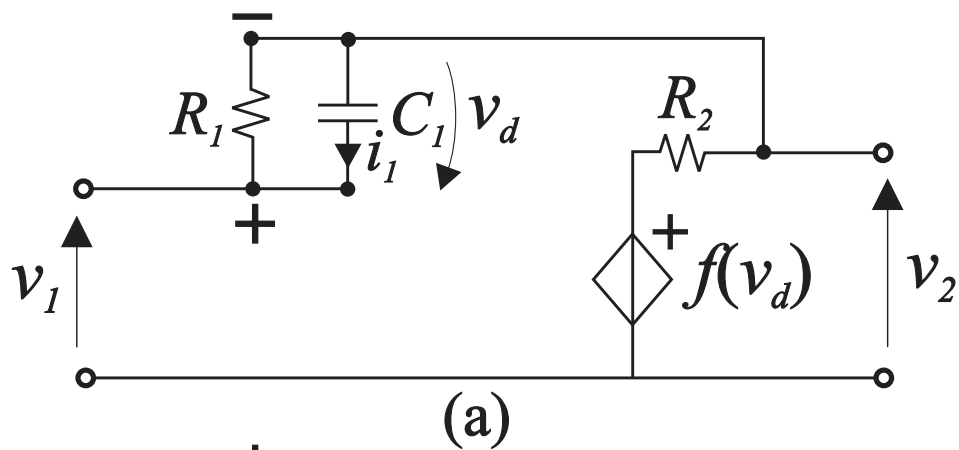- Modello dinamico: ((a) stabile, (b) instabile)



- Equazioni del modello dinamico a):

$$\begin{cases} \frac{v_2(t) - f(v_d(t))}{R_2} + \frac{v_2(t) - v_1(t)}{R_1} - C_1 \frac{dv_d(t)}{dt} = 0 \\ v_d(t) = v_1(t) - v_2(t) \end{cases}$$

$$\frac{v_2(t) - f(v_1 - v_2)}{R_2} + \frac{v_2 - v_1}{R_1} + C_1 \frac{d(v_2 - v_1)}{dt} = 0$$

$$v_1(t) = V_1; \quad R_p = R_1 // R_2$$

$$\begin{cases} \frac{dv_2(t)}{dt} = -\frac{v_2(t)}{R_p C_1} + \frac{V_1}{R_1 C_1} + \frac{f(V_1 - v_2(t))}{R_2 C_1} \\ v_2(0) = V_1 - v_d(0) = V_1 - V_{d0} \end{cases}$$

$$V_1 = 0; R_2 \ll R_1 \Rightarrow R_2 \approx R_p; i_1 = -C_1 \frac{dv_2(t)}{dt}$$

$$\Rightarrow i_1 = \frac{v_2 - f(-v_2)}{R_p} = \frac{v_2 + f(v_2)}{R_p}$$

$$\text{se : } i_1 > 0 \Rightarrow \frac{dv_2(t)}{dt} < 0; \quad i_1 < 0 \Rightarrow \frac{dv_2(t)}{dt} > 0$$

- Equazioni del modello dinamico b):

$$\begin{cases} \frac{v_2(t) - f(v_d(t))}{R_2} + \frac{v_2(t) - v_1(t)}{R_1} + C_1 \frac{d(v_d(t))}{dt} = 0 \\ v_d(t) = v_2(t) - v_1(t) \end{cases}$$

$$\frac{v_2(t) - f(v_2 - v_1)}{R_2} + \frac{v_2 - v_1}{R_1} + C_1 \frac{d(v_2 - v_1)}{dt} = 0$$

$$v_1(t) = V_1; \quad R_p = R_1 // R_2$$


$$\begin{cases} \frac{dv_2(t)}{dt} = -\frac{v_2(t)}{R_p C_1} + \frac{V_1}{R_1 C_1} + \frac{f(v_2(t) - V_1)}{R_2 C_1} \\ v_2(0) = V_1 + v_d(0) = V_1 + V_{d0} \end{cases}$$

$$V_1 = 0; R_2 \ll R_1 \Rightarrow R_2 \approx R_p; i_1 = -C_1 \frac{dv_2(t)}{dt}$$


$$\Rightarrow i_1 = \frac{v_2 - f(v_2)}{R_p} = \frac{v_2 - f(v_2)}{R_p}$$

$$\text{se : } i_1 > 0 \Rightarrow \frac{dv_2(t)}{dt} < 0; \quad i_1 < 0 \Rightarrow \frac{dv_2(t)}{dt} > 0$$

- La dynamic route nei due casi è:

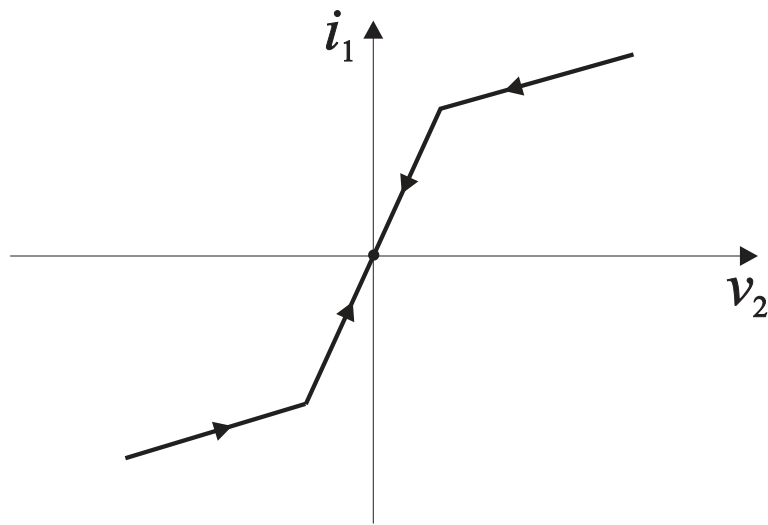

(a)

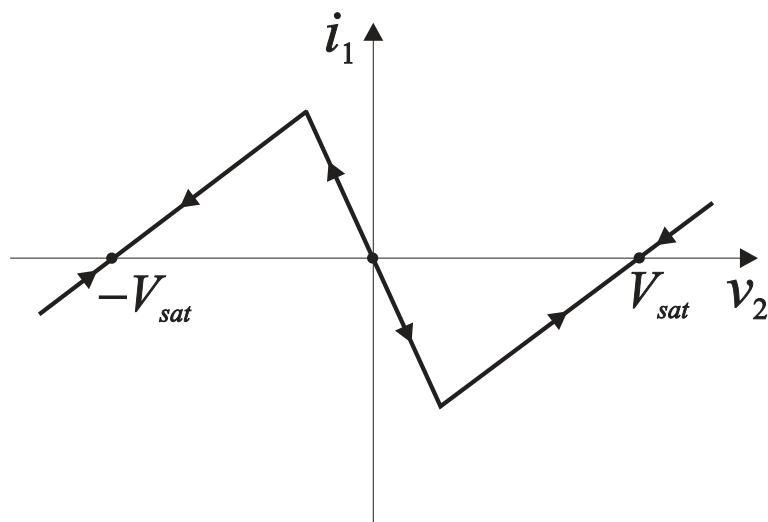

(b)

- Caso a): 1 punto stabile nell'origine
- Caso b): 1 punto instabile nell'origine e 2 punti stabili sugli assi

- Caso a)
- Transitorio per $V_1 = 0$ ($R_2 \cong R_p$; $C_1 R_p = \tau$):

$$\begin{cases} \frac{dv_2(t)}{dt} = -\frac{v_2(t)}{\tau} + \frac{f(-v_2(t))}{\tau} = -\frac{v_2(t)}{\tau} - \frac{f(v_2(t))}{\tau} \\ v_2(0) = V_{20} (= -V_{d0}); V_{20} > V_A; t \geq 0 \end{cases}$$

$$\frac{dv_2(t)}{dt} = -\frac{v_2(t)}{\tau} - \frac{V_{sat}}{\tau}$$

$$\Rightarrow \begin{cases} v_2(t) = [V_{20} + V_{sat}] e^{-\frac{t}{\tau}} - V_{sat} \\ t \geq 0, v_2(t) \geq V_A \end{cases}$$



$$v_2(t_A) = V_A = [V_{20} + V_{sat}] e^{-\frac{t_A}{\tau}} - V_{sat}$$

$$\Rightarrow t_A = -\tau \ln \left(\frac{V_A + V_{sat}}{V_{20} + V_{sat}} \right) \Rightarrow \Delta t = t - t_A$$

$$\begin{cases} \frac{dv_2(\Delta t)}{dt} = -\frac{v_2(\Delta t)}{\tau} - \frac{Av_2(\Delta t)}{\tau} = -\frac{v_2(\Delta t)}{\tau} (1 + A) \\ v_2(0) = V_A; \Delta t \geq 0 \end{cases}$$

$$\Rightarrow \begin{cases} v_2(t - t_A) = V_A e^{-\frac{(t-t_A)}{\tau}(1+A)} \\ t \geq t_A \end{cases}$$

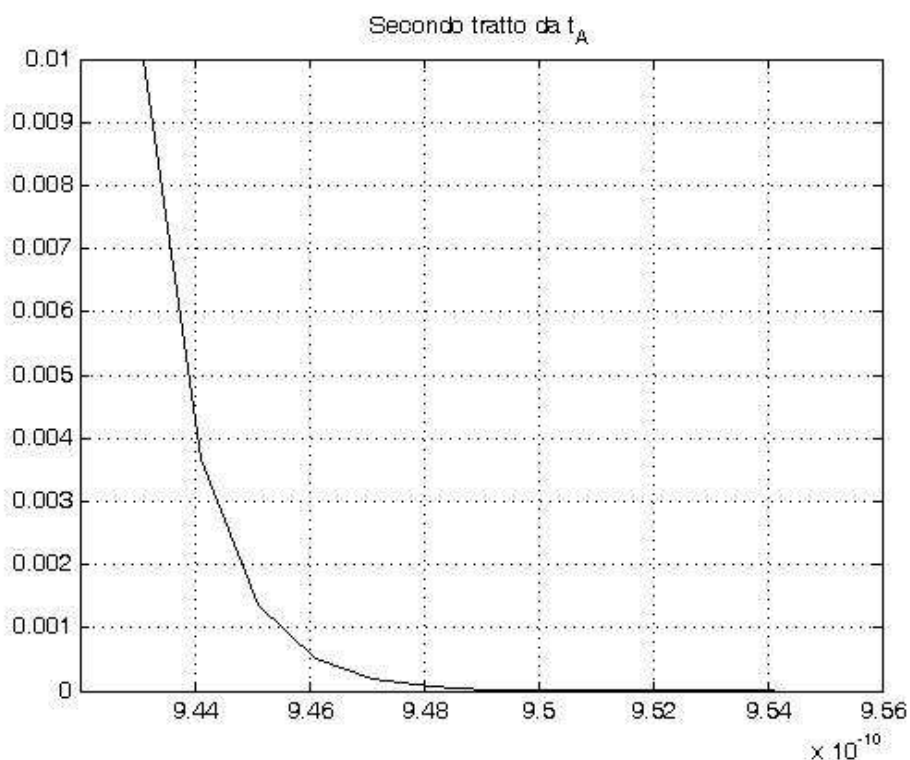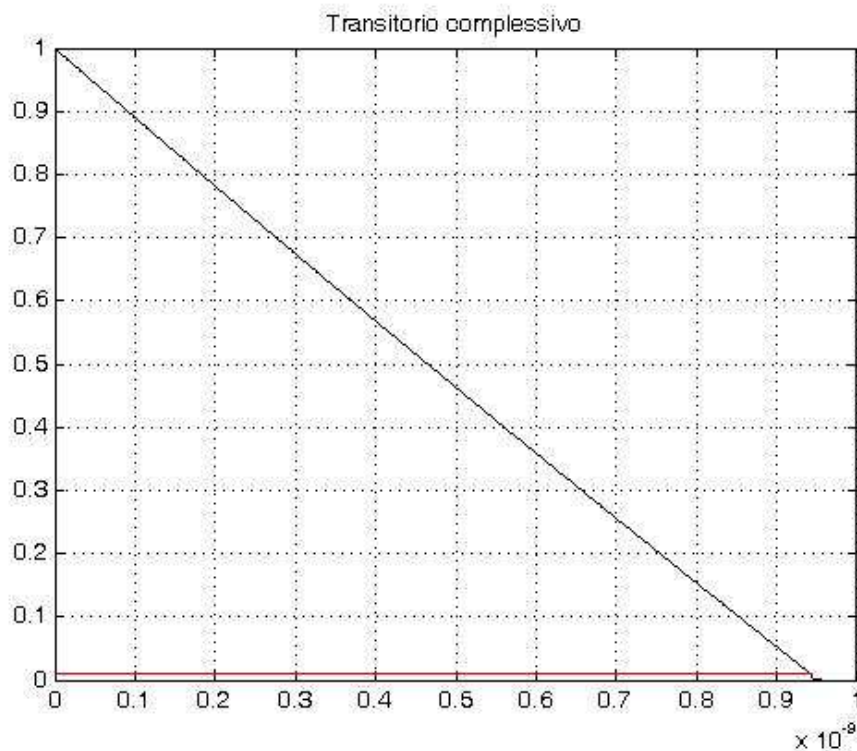- Caso a): esempio di transitorio per:
- $A = 10'000$; $V_{sat} = 10$; $V_A = 0.01$, $V_{20} = 1$;
 $C = 1\text{nF}$, $R_p = 10\ \Omega$; $\tau = 10^{-8} \Rightarrow t_A = 9.4 \cdot 10^{-10}$



- Caso b)
- Transitorio per $V_1 = 0$ ($R_2 \cong R_p$; $C_1 R_p = \tau$):

$$\begin{cases} \frac{dv_2(t)}{dt} = -\frac{v_2(t)}{\tau} + \frac{f(v_2(t))}{\tau} \\ v_2(0) = V_{20}(= V_{d0}); 0 < V_{20} < V_A; t \geq 0 \end{cases}$$

$$\begin{aligned} \frac{dv_2(t)}{dt} &= -\frac{v_2(t)}{\tau} + \frac{Av_2(t)}{\tau} = \frac{v_2(t)}{\tau} (A - 1) \\ \Rightarrow \begin{cases} v_2(t) = V_{d0} e^{\frac{t}{\tau}(A-1)} \\ t \geq 0, v_2(t) \leq V_A \end{cases} \end{aligned}$$

$$v_2(t_A) = V_A = V_{d0} e^{\frac{t_A}{\tau}(A-1)} \Rightarrow t_A = \frac{\tau}{A-1} \ln\left(\frac{V_A}{V_{d0}}\right)$$

$$\Delta t = t - t_A \Rightarrow \begin{cases} \frac{dv_2(\Delta t)}{d\Delta t} = -\frac{v_2(\Delta t)}{\tau} + \frac{V_{sat}}{\tau} \\ v_2(0) = V_A; \Delta t \geq 0 \end{cases}$$

$$\Rightarrow \begin{cases} v_2(t - t_A) = [V_A - V_{sat}] e^{-\frac{(t-t_A)}{\tau}} + V_{sat} \\ t \geq t_A \end{cases}$$

- Caso b): esempio di transitorio per:
- $A = 10'000$; $V_{sat} = 10$; $V_A = 0.01$, $V_{20} = 0.001$;
 $C = 1\text{nF}$, $R_p = 10\ \Omega$; $\tau = 10^{-8} \Rightarrow t_A = 2.3 \cdot 10^{-12}$

