

Introduzione alle FPGA

Lab 2

Prof. Laura Gonella

Laboratorio di Acquisizione e Controllo Dati
a.a. 2024-25

Examples and exercises

- Example: OR gate
 - Exercise 1: AND gate
 - Exercise 2: 2to1 MUX
-

- Example: OR gate with “process”
 - Example: D-FF
 - Exercise 3: 2to1 MUX with “process” and “if” statement
-

- Exercise 4: D-FF with synchronous reset
- Exercise 5: Shift register


process statement

- The **process** statement is used in VHDL to define blocks to be evaluated sequentially
 - **Statements inside a process are evaluated sequentially** (like most programming languages)
 - **Multiple process blocks are evaluated concurrently**
- A process can have a sensitivity list
 - List of signal to which the process is sensitive (for example a clock)
 - **The process is executed only when there is a change to a signal in the sensitivity list**
- Processes are used to define a block of combinational logic or a block of sequential logic – the latter is far more used

```
<process_name> : process (signalA , signalB )  
begin  
    statement 1;  
    statement 2;  
    ...  
    statement N;  
end process <process_name >;
```

 Example: OR gate with process statement

```
design.vhd +
1 -- Simple OR gate design
2 library IEEE;
3 use IEEE.std_logic_1164.all;
4
5 entity or_gate is
6 port(
7   a: in std_logic;
8   b: in std_logic;
9   q: out std_logic);
10 end or_gate;
11
12 architecture rtl of or_gate is
13   signal or_g1 : std_logic;
14 begin
15   or_g1 <= a or b;
16   q <= or_g1;
17 end rtl;
```





```
design.vhd +
1 -- Simple OR gate design
2 library IEEE;
3 use IEEE.std_logic_1164.all;
4
5 entity or_gate is
6 port(
7   a: in std_logic;
8   b: in std_logic;
9   q: out std_logic);
10 end or_gate;
11
12 architecture rtl of or_gate is
13 begin
14   process(a, b) is
15   begin
16     q <= a or b;
17   end process;
18 end rtl;
```

Could have been written as:

```
architecture rtl of or_gate is
begin
    q <= a or b;
end rtl
```

  Example of sequential logic with process: D-FF design

```
1  -- Code your design here
2
3  library IEEE;
4  use IEEE.std_logic_1164.all;
5
6  entity DFF is
7  port(
8      D      : in  std_logic;
9      CLK    : in  std_logic;
10     Q      : out std_logic);
11 end DFF;
12
13 architecture rtl of DFF is
14 begin
15     process (CLK)
16     begin
17         if rising_edge(CLK) then
18             Q <= D;
19         end if;
20     end process;
21 end rtl;
```



Edge detection

```
1  -- Code your design here
2
3  library IEEE;
4  use IEEE.std_logic_1164.all;
5
6  entity DFF is
7  port(
8      D    : in  std_logic;
9      CLK  : in  std_logic;
10     Q    : out std_logic);
11 end DFF;
12
13 architecture rtl of DFF is
14 begin
15     process (CLK)
16     begin
17         if rising_edge(CLK) then
18             Q <= D;
19         end if;
20     end process;
21 end rtl;
```

- **process** block

- In this example, the sensitivity list contains the clock signal, CLK
 - The process is executed only when there is a change to the clock

- **rising_edge(CLK)**

- **functions to detect signal and clock edges** in the `ieee.std_logic_1164.all` package
- **rising_edge(s)** returns true, if there is a rising edge on the signal `s`
- **falling_edge(s)** returns true, if there is a falling edge on the signal `s`

Conditional statement: if

- Conditional statement: **if**

- Conditional execution inside a process
- Condition should return a Boolean (true/false)
- Keywords: **if, elsif, and else**

```
1  -- Code your design here
2
3  library IEEE;
4  use IEEE.std_logic_1164.all;
5
6  entity DFF is
7  port(
8      D    : in  std_logic;
9      CLK  : in  std_logic;
10     Q    : out std_logic);
11 end DFF;
12
13 architecture rtl of DFF is
14 begin
15     process (CLK)
16     begin
17         if rising_edge(CLK) then
18             Q <= D;
19         end if;
20     end process;
21
22 end rtl;
23
24
25
26
```

```
if <condition1> then
    <vhdl statement>;
end if;
```

```
if <condition1> then
    <vhdl statement 1>;
else
    <vhdl statement 2>;
end if;
```

```
if <condition1> then
    <vhdl statement 1>;
elsif <condition2> then
    <vhdl statement 2>;
else
    <vhdl statement 3>;
end if;
```

Conditional statement: if

- Conditional statement: **if**

```
1  -- Code your design here
2
3  library IEEE;
4  use IEEE.std_logic_1164.all;
5
6  entity DFF is
7  port(
8      D   : in  std_logic;
9      CLK :in  std_logic;
10     Q   : out std_logic);
11 end DFF;
12
13 architecture rtl of DFF is
14 begin
15     process (CLK)
16     begin
17         if rising_edge(CLK) then
18             Q <= D;
19         end if;
20     end process;
21 end rtl;
```

Relational operators:

=	equal
/=	not equal
<	less than
<=	less than or equal
>	greater than
>=	greater than or equal

Logical operators:

not <i>a</i>	true if <i>a</i> is false
<i>a</i> and <i>b</i>	true if <i>a</i> and <i>b</i> are true
<i>a</i> or <i>b</i>	true if <i>a</i> or <i>b</i> are true
<i>a</i> nand <i>b</i>	true if <i>a</i> or <i>b</i> is false
<i>a</i> nor <i>b</i>	true if <i>a</i> and <i>b</i> are false
<i>a</i> xor <i>b</i>	true if exactly one of <i>a</i> or <i>b</i> are true
<i>a</i> xnor <i>b</i>	true if <i>a</i> and <i>b</i> are equal

Example of sequential logic with process: D-FF testbench

- Library

- Entity (empty)

- Architecture

- Declarative part
 - Component declaration
 - Signal declaration
- Implementation part
 - Component instantiation
 - Clock generation process
 - Stimulus process

```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3
4 entity TB_DFF is
5   -- empty
6 end TB_DFF;
7
8 architecture behavioral of TB_DFF is
9
10  -- Component declaration of the D Flip-Flop
11  component DFF is
12    port(
13      D : in std_logic;
14      CLK : in std_logic;
15      Q : out std_logic);
16  end component;
17
18  -- Signals to connect to the D flip-flop
19  signal D : STD_LOGIC := '0';
20  signal CLK : STD_LOGIC := '0';
21  signal Q : STD_LOGIC;
22
23  signal StopClock : BOOLEAN; -- boolean number (true or false)
24  constant Period : TIME := 10 ns; -- constant
25
26 begin
27
28  -- Instantiate the D flip-flop
29  DUT: DFF port map(D, CLK, Q);
30
31  -- Clock generation process
32  ClockGenerator: process
33  begin
34    while not StopClock loop
35      Clk <= '0';
36      wait for Period/2;
37      Clk <= '1';
38      wait for Period/2;
39    end loop;
40    wait;
41  end process ClockGenerator;
42
43  -- Stimulus process
44  stim_proc: process
45  begin
46    d <= '0';
47    wait for 20 ns;
48
49    d <= '1';
50    wait for 20 ns;
51
52    d <= '0';
53    wait for 20 ns;
54
55    d <= '1';
56    wait for 20 ns;
57
58    StopClock <= True;
59
60    wait;
61  end process stim_proc;
62
63 end behavioral;
```

Constants in VHDL

```
11
12 architecture behavioral of TB_DFF is
13
14 -- Component declaration of the D Flip-Flop
15 component DFF is
16   port(
17     D   : in  std_logic;
18     CLK : in  std_logic;
19     Q   : out std_logic);
20 end component;
21
22 -- Signals to connect to the D flip-flop
23   signal D   : STD_LOGIC := '0';
24   signal CLK : STD_LOGIC := '0';
25   signal Q   : STD_LOGIC;
26
27   signal StopClock : BOOLEAN; -- boolean number (true or false)
28   constant Period : TIME := 10 ns; -- constant
29
30 begin
```

Architecture – Declarative part

- Component declaration
- Signals declaration
- Note the signals and constant to be used for the clock generation process

constant

- Can be defined in **process**, **architecture** or **package** blocks
- **:=** assignment operator for constants

Clock simulation

Signals and constant for clock generation process defined in the declarative part of the architecture

```
24 | signal CLK : STD_LOGIC := '0';
27 | signal StopClock : BOOLEAN; -- boolean number (true or false)
28 | constant Period : TIME := 10 ns; -- constant
```

```
30 | begin
31 |
32 | -- Instantiate the D flip-flop
33 | DUT: DFF port map(D, CLK, Q);
34 |
35 | -- Clock generation process
36 | ClockGenerator: process
37 | begin
38 | while not StopClock loop
39 |   Clk <= '0';
40 |   wait for Period/2;
41 |   Clk <= '1';
42 |   wait for Period/2;
43 | end loop;
44 | wait;
45 | end process ClockGenerator;
```

```
46 |
47 | -- Stimulus process
48 | stim_proc: process
49 | begin
50 |
51 |   d <= '0';
52 |   wait for 20 ns;
53 |
54 |   d <= '1';
55 |   wait for 20 ns;
56 |
57 |   d <= '0';
58 |   wait for 20 ns;
59 |
60 |   d <= '1';
61 |   wait for 20 ns;
62 |
63 |   StopClock <= True;
64 |   wait;
65 |
66 | end process stim_proc;
67 |
68 |
69 | end behavioral;
```

Architecture – Implementation part

- Component instantiation
- Clock generation process
 - Simple to define in testbenches
 - Can be running indefinitely or for a finite number of clock cycles
 - In this example, we use the signal **StopClock** to stop the clock

Clock simulation

Signals and constant for clock generation process defined in the declarative part of the architecture

```
24 | signal CLK : STD_LOGIC := '0';  
27 | signal StopClock : BOOLEAN; -- boolean number (true or false)  
28 | constant Period : TIME := 10 ns; -- constant
```

```
30 | begin  
31 |  
32 | -- Instantiate the D flip-flop  
33 | DUT: DFF port map(D, CLK, Q);  
34 |  
35 | -- Clock generation process  
36 | ClockGenerator: process  
37 | begin  
38 | while not StopClock loop  
39 |   Clk <= '0';  
40 |   wait for Period/2;  
41 |   Clk <= '1';  
42 |   wait for Period/2;  
43 | end loop;  
44 | wait;  
45 | end process ClockGenerator;
```

```
46 |  
47 | -- Stimulus process  
48 | stim_proc: process  
49 | begin  
50 |  
51 |   d <= '0';  
52 |   wait for 20 ns;  
53 |  
54 |   d <= '1';  
55 |   wait for 20 ns;  
56 |  
57 |   d <= '0';  
58 |   wait for 20 ns;  
59 |  
60 |   d <= '1';  
61 |   wait for 20 ns;  
62 |  
63 |   StopClock <= True;  
64 |   wait;  
65 |  
66 | end process stim_proc;  
67 |  
68 |  
69 | end behavioral;
```

Architecture – Implementation part

- Component instantiation
- Clock generation process
 - Examples of clock generation syntax

```
architecture behavior of testbench is  
  signal clk : std_logic := '0';  
begin  
  clk <= not clk after 5 ns;  
end behavior;
```

```
architecture behavior of testbench is  
  signal clk : std_logic := '0';  
  constant CLK_PERIOD : time := 10 ns;  
begin  
  clk <= not clk after CLK_PERIOD/2;  
end behavior;
```

```
architecture behavior of testbench is  
  signal clk : std_logic := '0';  
  constant NCYCLES : integer := 100;  
begin  
  clk_proc : process  
  begin  
    for I in 0 to NCYCLES-1 loop  
      clk <= not clk;  
      wait for 5 ns;  
      clk <= not clk;  
      wait for 5 ns;  
    end loop;  
    wait;  
  end process;  
end behavior;
```

while and for statements

while statement

- Repeats a block of code as long as the condition is true.
- The condition is evaluated before each iteration.
- Used for loops where the number of iterations is not known beforehand.

```
while <condition> loop  
    <sequential statements>  
end loop;
```

for statement

- Repeats a block of code a fixed number of times.
- The loop variable automatically iterates over the specified range.
- Used when the number of iterations is known beforehand.

```
for <loop_variable> in <range> loop  
    <sequential statements>  
end loop;
```

Example of sequential logic with process: D-FF simulation waveforms



if vs when/else

- VHDL is a concurrent language, it provides two different solutions to implement a conditional statement:
 - **Sequential** conditional statement: **if**
 - **Concurrent** conditional statement: **when/else**
- The **sequential** conditional statement can be used in **process**
- The **concurrent** conditional statement can be used in the architecture concurrent section, i.e. between the **begin/end** section of the VHDL architecture definition
- Total equivalence between **if** sequential statement and **when/else** statement; either can be used
- When using a conditional statement, one must pay attention to the final hardware implementation
 - A conditional statement can be translated into a MUX or a comparator or a huge amount of combinatorial logic

Exercise 3: MUX 2to1 code


- Rewrite the MUX example using **process** and the **if** statement

End of part 2

- process statement
- Edge detection
- Conditional statement: if
- Constants in VHDL
- Clock simulation
- while and for statements
- Example: OR gate with “process”
- Example: D-FF
- Exercise 3: 2to1 MUX with “process” and “if” statement


Reset signal

 - Typically the D-FF have an input for the reset signal
- Upon application of the reset $Q = 0, \bar{Q} = 1$
- The reset signal can be **synchronous** or **asynchronous** to the process clock




```
process(CLK, RESET)
begin
  if RESET = '1' then
    Q <= '0';
  elsif rising_edge(CLK) then
    Q <= D;
  end if;
end process;
```

 -- Asynchronous reset: Reset Q to '0'
-- On rising clock edge, transfer D to Q



```
process(CLK, RESET)
begin
  if rising_edge(CLK) then
    if RESET = '1' then
      Q <= '0';
    else
      Q <= D;
    end if;
  end if;
end process;
```


-- Synchronous reset: Reset Q to '0'
-- On rising clock edge, transfer D to Q

 

Exercise 4: Design and simulate a D-FF with synchronous reset

 Exercise 5: Design and simulate a shift register

- Design and simulate a shift register made of 4 D-FF with serial input, serial output



Assigning vectors

```
signal vec : std_logic_vector(7 downto 0) := (others => '0'); -- vec is 00000000
vec <= "10100000"; -- vec is now 10100000
vec(0) <= '1'; -- vec is now 10100001
vec(2 downto 1) <= "01"; -- vec is now 10100011
vec(7 downto 5) <= vec(2 downto 0); -- vec is now 01100011
```

End of part 3

- Reset signal (synch, asynch)
- Assigning vectors
- Exercise 4: D-FF with synchronous reset
- Exercise 5: Shift register

Resources

- [NANDLAND](#)
- [fpga4fun](#)
- Free range VHDL [book](#)