



**UNIVERSITÀ  
DEGLI STUDI  
DI TRIESTE**



Dipartimento di

**Fisica**

Dipartimento d'Eccellenza 2023-2027

# **VHDL Part 2**

---

Laboratorio di acquisizione e controllo dati

UniTs a.a. 2025-2026

# Models in VHDL architecture

---

- The behavior of the digital circuit is modelled in the VHDL architecture through concurrent statements
- There are three main approaches to model a circuit in VHDL architecture
  - **Data-flow** style
  - **Behavioral** style
  - **Structural** style (not for this course)

# Data flow style

---

- Describes the circuit as a **representation of how the data flows in it**
- Statements describe the relationship between **input** and **output** signals with VHDL **operators** (e.g. AND, OR, NOT)
- Uses **concurrent, conditional, selected** signal assignment statements
- All the exercises seen up to now are data flow style architectures
- Works well for **small circuits** where you have an **idea of the underlying hardware**

# Behavioral style

---

- Higher circuit abstraction level
- Models how the **circuit should behave**
- Leaves the details of the **implementation** to the **synthesis tool**
- Used for **complex circuits**
- Uses **process** statement

# Process statement

---

```
-- PROCESS STATEMENT
-- Within a process statement, all statements are executed sequentially
-- The process itself is a concurrent statement and will be executed concurrently with other concurrent statements in the architecture
-- The process statement is used when some commands need to be executed in a sequential manner

-- Process has an identifier, a sensitivity list, a declaration part and an implementation part containing sequential statements
-- Syntax for process statement
<identifier> : process (sensitivity_list) is
    <item_declaration>
begin
    <sequential_statements>
end process <identifier>;
```

# Data flow vs behavioral

```
1  -- EXAMPLE: OR GATE DATA FLOW MODEL
2
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5
6  entity or_gate_df is
7  Port (
8      A : in STD_LOGIC;
9      B : in STD_LOGIC;
10     Y : out STD_LOGIC
11 );
12 end or_gate_df;
13
14 architecture dataflow of or_gate_df is
15
16 begin
17     Y <= A or B;
18     -- concurrent signal assignment statement
19     -- the statement in the data flow style architecture is re-evaluated any time there is a change in signal A or signal B
20
21 end dataflow;
22
23
24 -- EXAMPLE: OR GATE BEHAVIORAL MODEL
25
26 library IEEE;
27 use IEEE.STD_LOGIC_1164.ALL;
28
29 entity or_gate_b is
30 Port (
31     A : in STD_LOGIC;
32     B : in STD_LOGIC;
33     Y : out STD_LOGIC
34 );
35 end or_gate_b;
36
37 architecture behavioral of or_gate_b is
38
39 begin
40
41     or_proc: process (A,B) is
42     begin
43         Y <= A or B;
44         -- sequential signal assignment statement
45         -- same syntax as of the concurrent signal assignment statement
46         -- it is sequential because it appears inside a process statement
47         -- execution of the statement in the behavioral style architecture is controlled by which signals appear in the process sensitivity list
48     end process or_proc;
49
50 end behavioral;
```

# Sequential statements

---

- There are three types of sequential statements
  - **Sequential** signal assignment statement (see previous slide)
  - **if** statement
  - **case** statement

# if statement

---

```
-- IF STATEMENT
-- Sequential equivalent of the conditional signal assignment statement

-- A sequence of statements is executed if an associated condition is true
-- Depending on the conditions, the statements associated with one or none of the branches is executed

-- Syntax for if statement
if <condition> then
  <statements>
elsif <condition> then
  <statements>
else
  <statements>
-- the final "else" clause does not have an associated "then" keyword
-- the final "else" clause is an optional catch-all
-- if none of the previous conditions is evaluated as true, then this statement is executed
-- unless you want to implement a memory function, you must use the else clause!!!
-- we will discuss this more in the D-FF exercise

end if;
```

# case statement

---

```
-- CASE STATEMENT
-- sequential equivalent of the selected signal assignment statement

-- a sequence of statements is executed if an associated expression is true
-- the assignment is made depending upon the value of the single control expression
-- only one set of sequential statements is executed for each execution of the case statement
-- the statements executed are determined by the first when branch to evaluate as true

case <expression> is
  when <choices> =>
    <sequential_statements>
  when <choices> =>
    <sequential_statements>
  when others =>
    <sequential_statements>
    -- "when others" is an optional catch-all, but it is good practice to include it
end case;
```


# VHDL for sequential circuits

---

- All examples seen so far are **combinational** circuits
  - They produce outputs based **only on the current inputs**
- A **sequential** circuit is a type of digital logic circuit whose output depends not only on the **current inputs** but also on the **previous states** of the circuit
  - Sequential circuits have **memory elements** (e.g. flip-flop) that store information about previous states
  - They are often controlled by a **clock signal** that synchronizes state changes
- In VHDL sequential circuits are typically modelled with **behavioral style** architecture
  - In general, a certain logic circuit can be modelled in different ways, that will result in the same hardware
  - But for synchronous memory elements, behavioral style is the optimal method
 
# D-FF

```
1  -- EXAMPLE: D-FF
2
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5
6  entity d_flip_flop is
7      Port (
8          clk : in  STD_LOGIC;
9          d   : in  STD_LOGIC;
10         q   : out STD_LOGIC
11     );
12 end d_flip_flop;
13
14 architecture Behavioral of d_flip_flop is
15
16 begin
17     process(clk)
18         -- the statements within process are executed every time there is a change in the logic level of clk
19     begin
20         if rising_edge(clk) then
21             -- "rising_edge()" is a VHDL function
22             -- changes in the circuit happen only on the rising egde of the clk input
23
24             -- THIS WAY OF WRITING THE CODE IS WHAT MAKES THE D-FF OUTPUT SYNCHRONOUS TO THE CLOCK INPUT!!! ---
25
26             q <= d;
27         end if;
28         -- a condition that indicates what should happen if the listed if condition is not met, is not provided
29         -- if the if condition is not met, the D-FF does not chnage the value of q
30         -- the D-FF must remember the current value
31         -- THIS IS THE WAY TO INDUCE MEMORY IN VHDL!!!
32     end process;
33
34 end Behavioral;
35
```



# Test bench of D-FF

```
1  -- EXAMPLE: TEST BENCH OF D-FF
2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4
5  entity d_flip_flop_tb is
6  end d_flip_flop_tb;
7
8  architecture Behavioral of d_flip_flop_tb is
9
10     -- Component declaration
11     component d_flip_flop
12     Port (
13         clk : in  STD_LOGIC;
14         d   : in  STD_LOGIC;
15         q   : out STD_LOGIC
16     );
17     end component;
18
19     -- Testbench signals
20     signal clk_tb      : STD_LOGIC := '0';
21     signal d_tb       : STD_LOGIC := '0';
22     signal q_tb       : STD_LOGIC;
23     signal stop_clock_tb : BOOLEAN := false; -- note BOOLEAN type, not seen before
24
25     -- Clock period constant
26     constant CLK_PERIOD : time := 10 ns;
27     -- synthax for constant declaration
28     -- constant <name> : type := <initial value>;
29     -- "time" is a data type used in simulations
30     -- FPGA does not have the concept of time
31     -- the constant is given a value at declaration that cannot be changed afterwards
32
```

# Test bench of D-FF

```
33 begin
34
35     -- DUT instantiation
36     uut: d_flip_flop
37     port map (
38         clk => clk_tb,
39         d   => d_tb,
40         q   => q_tb
41     );
42
43     -- Clock generation
44     clk_process : process
45     begin
46         while not stop_clock_tb loop
47
48             clk_tb <= '0';
49             wait for CLK_PERIOD/2;
50             clk_tb <= '1';
51             wait for CLK_PERIOD/2;
52         end loop;
53         wait;
54     end process;
55
56     -- Stimulus process
57     stim_proc : process
58     begin
59
60         wait for 12 ns;
61         d_tb <= '1';
62
63         wait for 10 ns;
64         d_tb <= '0';
65
66         wait for 10 ns;
67         d_tb <= '1';
68
69         wait for 10 ns;
70         d_tb <= '0';
71
72         wait for 20 ns;
73         stop_clock_tb <= true; -- stop the clock
74
75         wait;
76     end process;
77
78 end Behavioral;
```

# Exercise 6


---

- Simulate the D-FF in EDA playground
 
# Exercise 7

---

- Write the code for a **D-FF** with **asynchronous reset** and simulate it in EDA playground




- Instructions
  - Use behavioral style architecture with process statement
  - Use the if statement
  - **For sequential logic, a process can have at most two signals in the sensitivity list**
    - **Clock and reset, if the reset is asynchronous**
    - **Clock, if there is no reset or the reset is synchronous**
 
# Exercise 8

---

- Write the code for a **D-FF** with **synchronous reset** and simulate it in EDA playground



- Instructions
  - Use behavioral style architecture with process statement
  - Use the if statement
    - Tip: if statements can be nested

# Component declaration

```
1 -- EXAMPLE: TEST BENCH OF D-FF
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity d_flip_flop_tb is
6 end d_flip_flop_tb;
7
8 architecture Behavioral of d_flip_flop_tb is
9
10 -- Component declaration
11 component d_flip_flop
12 Port (
13     clk : in  STD_LOGIC;
14     d   : in  STD_LOGIC;
15     q   : out STD_LOGIC
16 );
17 end component;
18
19 -- Testbench signals
20 signal clk_tb      : STD_LOGIC := '0';
21 signal d_tb       : STD_LOGIC := '0';
22 signal q_tb       : STD_LOGIC;
23 signal stop_clock_tb : BOOLEAN := false; -- note BOOLEAN type, not seen before
24
25 -- Clock period constant
26 constant CLK_PERIOD : time := 10 ns;
27 -- syntax for constant declaration
28 -- constant <name> : type := <initial value>;
29 -- "time" is a data type used in simulations
30 -- FPGA does not have the concept of time
31 -- the constant is given a value at declaration that cannot be changed afterwards
32
33 begin
34
35 -- DUT instantiation
36 uut: d_flip_flop
37 port map (
38     clk => clk_tb,
39     d   => d_tb,
40     q   => q_tb
41 );
42
43 -- Clock generation
44 clk_process : process
45 begin
46     while not stop_clock_tb loop -- we do not discuss the while loop construct in this course
47                                     -- refer to the suggested book
48         clk_tb <= '0';
49         wait for CLK_PERIOD/2;
50         clk_tb <= '1';
51         wait for CLK_PERIOD/2;
52     end loop;
53     wait;
54 end process;
55
56 -- Stimulus process
57 stim_proc : process
58 begin
59     wait for 12 ns;
60     d_tb <= '1';
61
62     wait for 10 ns;
63     d_tb <= '0';
64
65     wait for 10 ns;
66     d_tb <= '1';
67
68     wait for 10 ns;
69     d_tb <= '0';
70
71     wait for 20 ns;
72     stop_clock_tb <= true; -- stop the clock
73
74     wait;
75 end process;
76
77 end Behavioral;
```

- Here we have a module called “d\_flip\_flop\_tb”
- Within this module we use another module “d\_flip\_flop”
- To do this we used this syntax

```
-- Component declaration in the declarative region of your architecture
component <component_name>
port (
    <port_0_name> : <mode> <type>;
    ...
    <port_n_name> : <mode> <type>
);
end component;
```

```
-- Component instantiation in the implementation region of the architecture
<instantiation_name> : <component_name>
port map (
    <component_port_0_name> => <parent_module_signal>,
    ...
    <component_port_n_name> => <parent_module_signal>,
);
```

# Entity declaration

- We could have done the same (use a module within a module) with this syntax


```
-- Entity instantiation in the implementation region of the architecture
<instantiation_name>: entity work.<entity_name> -- work is a special keyword in VHDL
-- it always refers to the same library as the main module
-- main module and instantiated module should be in the same library

port map (
<entity_port_0_name> => <parent_module_signal>,
...
<entity_port_n_name> => <parent_module_signal>,
);
```

```
1 -- EXAMPLE: TEST BENCH OF D-FF
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity d_flip_flop_tb is
6 d_flip_flop_tb;
7
8 architecture Behavioral of d_flip_flop_tb is
9
10 -- Testbench signals
11 signal clk_tb      : STD_LOGIC := '0';
12 signal d_tb       : STD_LOGIC := '0';
13 signal q_tb       : STD_LOGIC;
14 signal stop_clock_tb : BOOLEAN := false; -- note BOOLEAN type, not seen before
15
16 -- Clock period constant
17 constant CLK_PERIOD : time := 10 ns;
18 -- synthax for constant declaration
19 -- constant <name> : type := <initial value>;
20 -- "time" is a data type used in simulations
21 -- FPGA does not have the concept of time
22 -- the constant is given a value at declaration that cannot be changed afterwards
23
24 begin
25
26 -- DUT instantiation
27 uut: entity work.d_flip_flop -- work is a special keyword in VHDL
28 -- it always refers to the same library as the main module
29 -- main module and instantiated module should be in the same library
30
31     port map (
32         clk => clk_tb,
33         d  => d_tb,
34         q  => q_tb
35     );
36
37 -- Clock generation
38 clk_process : process
39 begin
40     while not stop_clock_tb loop -- we do not discuss the while loop construct in this course
41         clk_tb <= '0';
42         wait for CLK_PERIOD/2;
43         clk_tb <= '1';
44         wait for CLK_PERIOD/2;
45     end loop;
46     wait;
47 end process;
48
49 -- Stimulus process
50 stim_proc : process
```
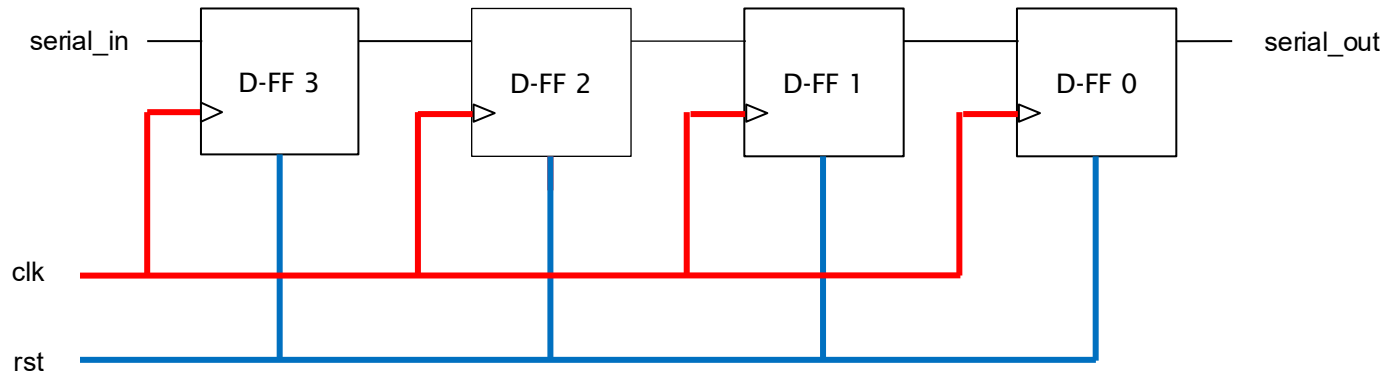
# Exercise 9

- Write the code for a **4-bit SISO shift register** in VHDL using D flip-flops, a clocked process, and asynchronous reset



- Instruction

- Syntax to access individual bit of a bus
  - `one_bit_signal <= my_bus(n)`
  - `one_bit_signal` gets the value of the  $n^{\text{th}}$  bit in the bus called `my_bus`

# Summary part 2

---

- VHDL modeling styles
  - **Data-flow** style
    - Uses concurrent, conditional, sequential signal assignment statements
  - **Behavioral** style
    - Uses process statements
- Process statements
  - Process is a concurrent statement
  - Statements appearing within process are sequential statements
- Sequential statements
  - **Sequential** signal assignment statement
  - **if** statement
  - **case** statement

# Summary part 2

---

- Sequential circuits are modelled with behavioral style architecture
- Memory is induced in VHDL by not specifying output conditions for every possible input condition
  - So, unless you want to model a memory, always specify all conditions
  - Unintended generation of memory is flagged by the synthesis tool
  - Memory adds complexity to the synthesized circuit
- Constants
  - Declared in **declarative** part of architecture
  - Constants are assigned a value at declaration that cannot be changed afterwards
  - This is done using the **assignment operator :=**

# Summary part 2

---

- Exercises
  - 6: D-FF
  - 7: D-FF with asynchronous reset
  - 8: D-FF with synchronous reset
  - 9: 4-bit SISO shift reset with asynchronous reset