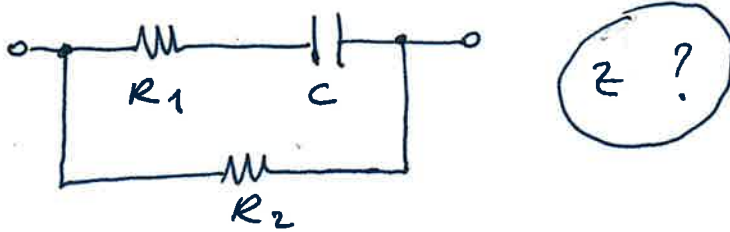


IMPEDENZA

①

①



$$Z_1 = R_1 + \frac{1}{j\omega C} = \frac{1 + j\omega C R_1}{j\omega C}$$

$$Z = \frac{Z_1 R_2}{Z_1 + R_2} = \frac{R_2 \frac{1 + j\omega C R_1}{j\omega C}}{R_2 + \frac{1 + j\omega C R_1}{j\omega C}} =$$

$$= \frac{R_2 (1 + j\omega C R_1)}{j\omega C R_2 + 1 + j\omega C R_1} = \frac{R_2 (1 + j\omega C R_1)}{1 + j\omega C (R_1 + R_2)}$$

$$\omega = 0 \Rightarrow Z \rightarrow R_2$$

$$\omega = \infty \Rightarrow Z \rightarrow \frac{R_1 R_2}{R_1 + R_2}$$

PROVENDO :

$$\omega = 2\pi f = 314 \text{ rad/s}$$

$$R_1 = 5 \Omega$$

$$R_2 = 10 \Omega$$


$$C = 1 \text{ mF}$$

$$Z_C = -j \frac{1}{\omega C} = -j 3.18 \Omega$$

$$Z_1 = 5 - j 3.18 \Omega$$

$$Z_2 = 0.92 - j 2.9 \Omega$$

(2)

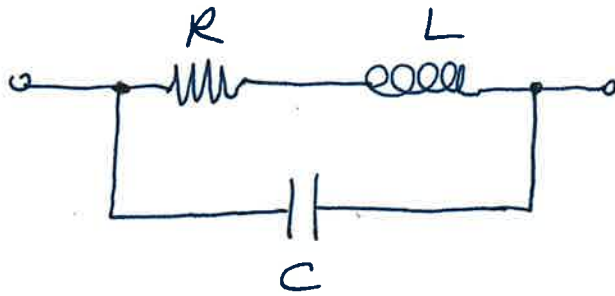 $\omega_0?$

$$Z_{RL} = R + j\omega L$$

$$Z = \frac{Z_{RL} \cdot Z_C}{Z_{RL} + Z_C} = \frac{(R + j\omega L) \frac{1}{j\omega C}}{(R + j\omega L) + \frac{1}{j\omega C}} =$$

$$= \frac{R + j\omega L}{1 + j\omega RC + (j\omega)^2 LC} =$$

$$= \frac{R + j\omega L}{(1 - \omega^2 LC) + j\omega RC} =$$

$$= \frac{(R + j\omega L)[(1 - \omega^2 LC) - j\omega RC]}{(1 - \omega^2 LC)^2 + (\omega^2 R^2 C^2)} =$$

$$= \frac{R(1 - \omega^2 LC) + \omega^2 R LC}{[DEN]} + j \frac{\omega L(1 - \omega^2 LC) - \omega R^2 C}{[DEN]}$$

$$X = \frac{\omega L(1 - \omega^2 LC) - \omega R^2 C}{[DEN]} = 0$$

$$L(1 - \omega^2 LC) = R^2 C$$

$$L - \omega^2 L^2 C = R^2 C$$

$$\omega^2 = \frac{L - R^2 C}{L^2 C}$$

$$\omega_0 = \sqrt{\frac{L - R^2 C}{L^2 C}}$$

$$\text{Re } R < \sqrt{L} \Rightarrow \omega_0 > 0$$

$$\omega \rightarrow 0 \Rightarrow Z \rightarrow R \quad ; \quad \omega \rightarrow \infty \Rightarrow Z \rightarrow 0$$

(3)

$$L - \omega^2 L^2 C - R^2 C = 0$$

$$\omega^2 L^2 C = L - R^2 C$$

$$\omega^2 = \sqrt{\frac{L - R^2 C}{L^2 C}}$$

$$L - R^2 C > 0$$

$$R^2 C < L$$

$$R < \sqrt{\frac{L}{C}}$$

$$R = \sqrt{\frac{L}{C}}$$

$$L - \omega^2 L^2 C - \frac{L}{C} C =$$

$$= -\omega^2 L^2 C < 0$$

$$X = 0 \text{ or } L - \omega^2 L^2 C - R^2 C = 0$$

$$-\omega^2 L^2 C + (L - R^2 C)$$

$$\text{or } R > \sqrt{\frac{L}{C}} \Rightarrow < 0$$

$$L - R^2 C < 0$$

$$\Rightarrow R^2 C > L$$

$$R > \sqrt{\frac{L}{C}}$$

```

% X di una impedenza risonante (R in serie con L)//(C)
close all;
R = 7;
C = 1e-3;
L = 0.1;

z0 = sqrt(L/C)
omega0 = sqrt((L-R*R*C)/(L*L*C))
omega = linspace(0, 1000, 1000);

zL = R + 1i*omega*L;
zC = 1 ./ (1i * omega * C);
zTotal = (zL.*zC)./(zL+zC);
plot(imag(zTotal))
grid;
xlabel('\omega [rad/s]');
ylabel('X [\Omega]');

```

